

# BALUNS AND FERRITES

Jacques Audet  
VE2AZX

[VE2AZX@amsat.org](mailto:VE2AZX@amsat.org)

Nov. 2006 Rev.1 June  
2008

VE2AZX

1

- REASONS FOR USING A BALUN
- TYPES OF BALUNS
- CHECK YOUR BALUN WITH AN SWR ANALYZER
- MESURING THE IMPEDANCE OF A NUMBER OF FERRITES
- IMPEDANCE MEASUREMENT RESULTS
- USING FERRITES ON A FEEDER AND HOUSE CONDUCTORS

## REASONS FOR USING A BALUN ?

BALUN = BALanced to Unbalanced - It's a transformer

Used to feed a balanced load, Ex: dipole


Decreases feeder radiation

The feed line becomes independent of the antenna:

We can change its length ... move it around

Without causing SWR change.

## REASONS FOR USING A BALUN ?

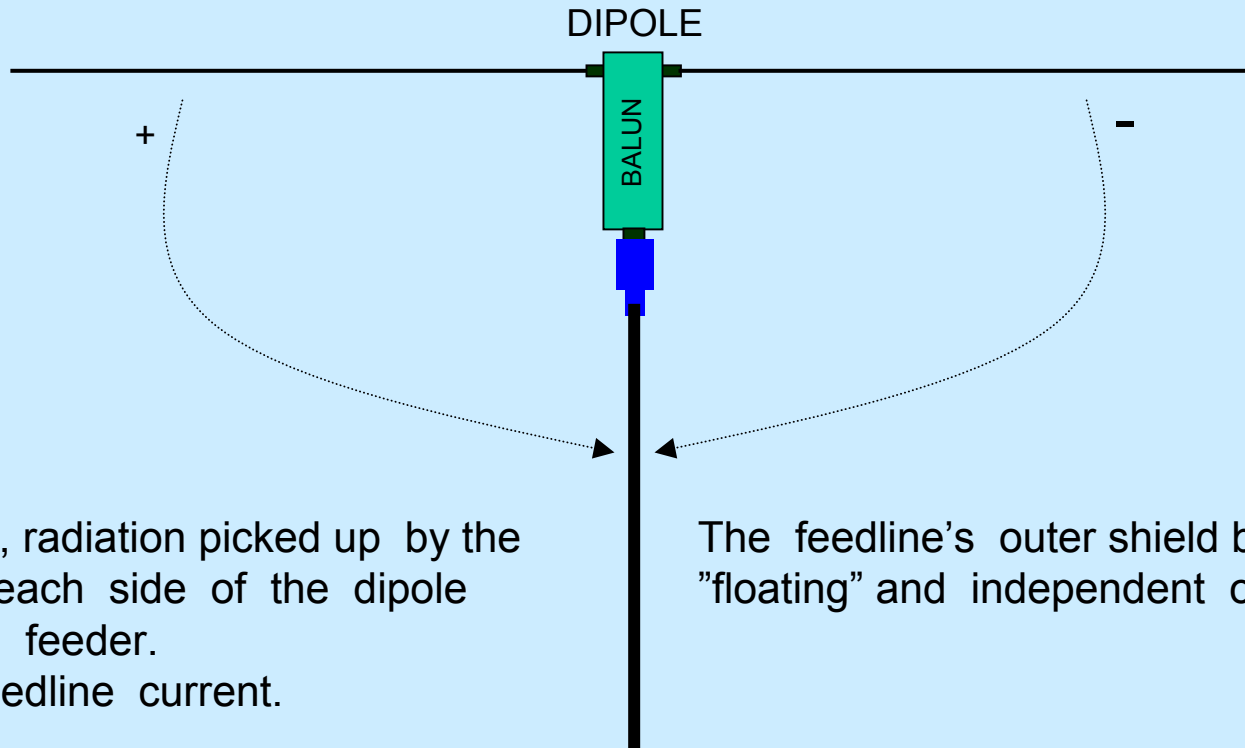

With a balun, radiation picked up by the feeder from each side of the dipole cancels at the feeder.  
Decreases feedline current.

The feedline's outer shield becomes "floating" and independent of the antenna.

The feedline should run away from the dipole at right angle.  
The dipole should be parallel to the ground.

A non symmetrical antenna Ex: Windom...  
Will require the use of a current balun

# BALUN TYPES

## VOLTAGE

- TRANSFORMER WITH WINDINGS GIVING A BALANCED OUTPUT
- IN-OUT IMPEDANCES ARE DETERMINED BY THE TURNS RATIO. A WIDE RANGE OF RATIOS IS POSSIBLE.
- OPERATES OVER A SOMEWHAT LIMITED BANDWIDTH (100 TO 1)


## CURRENT

- USES TRANSMISSION LINES WOUND ON A CORE
- MAY USE A COAXIAL CABLE OR A PARALLEL WIRE LINE WITH OR WITHOUT FERRITES.
- COMMON IMPEDANCE RATIOS: 1:1 AND 4:1
- OPERATE OVER A MUCH WIDER BAND OF FREQUENCIES

# 1:1 VOLTAGE BALUN

- 3 IDENTICAL WINDINGS


- GENERALLY 50 : 50 ohms

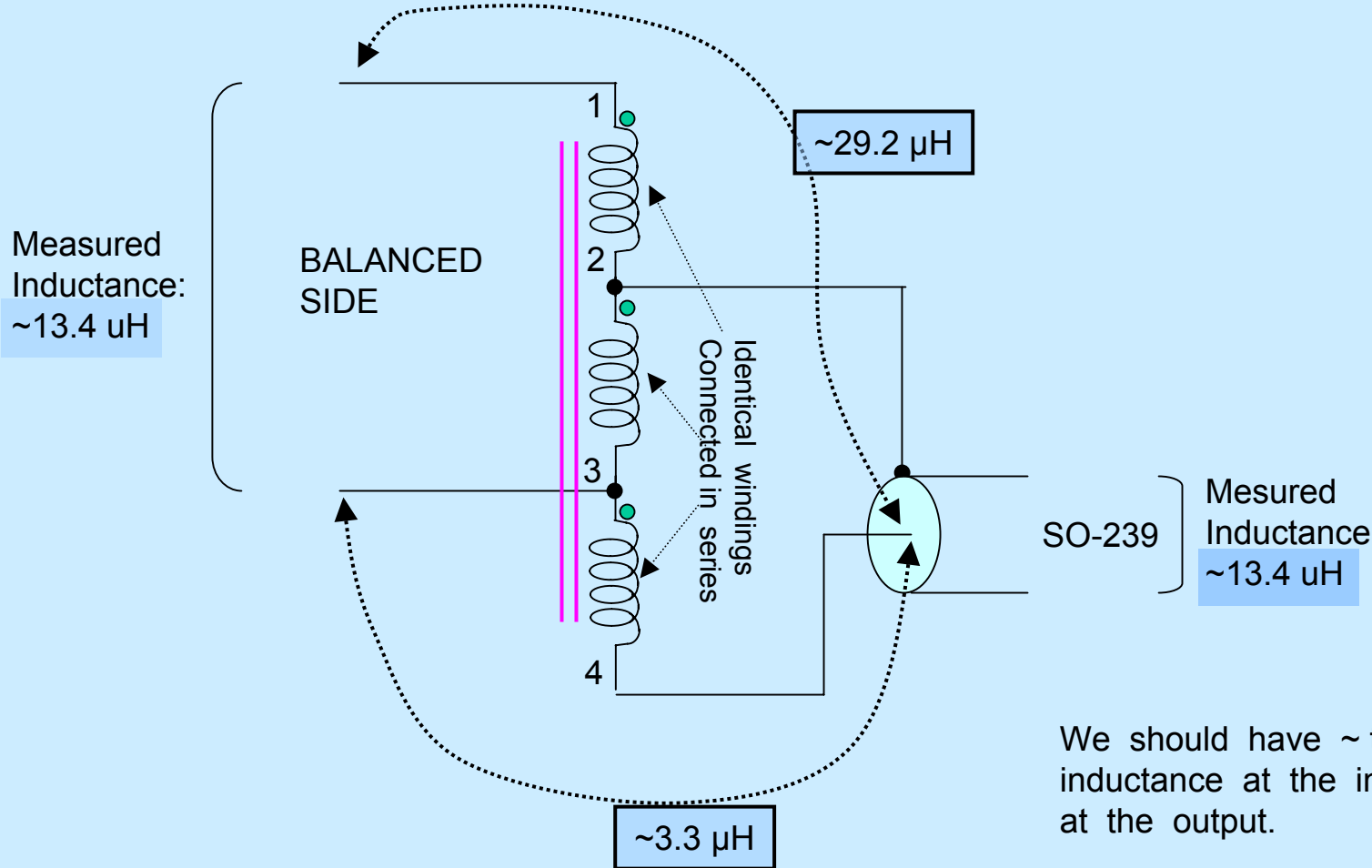

We should have ~ the same inductance at the input and at the output.

# VOLTAGE BALUN 4:1

- 2 IDENTICAL WINDINGS


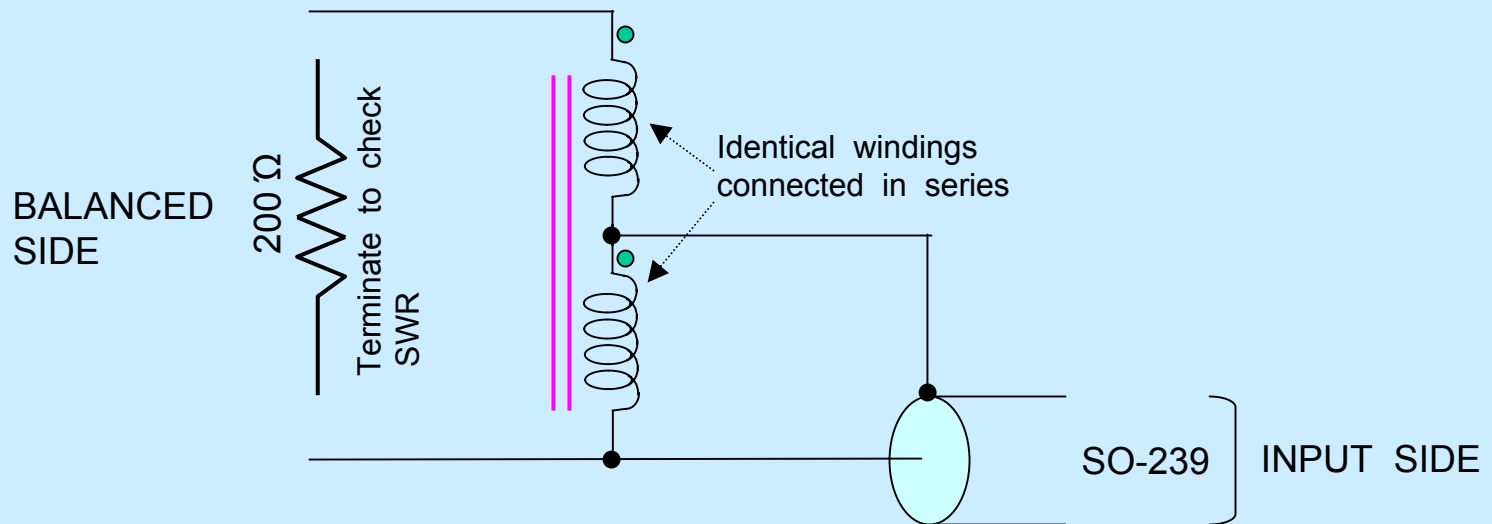


The measured inductance at the output is ~ 4X the input inductance as a result of inductance coupling.
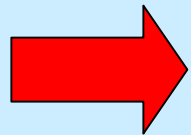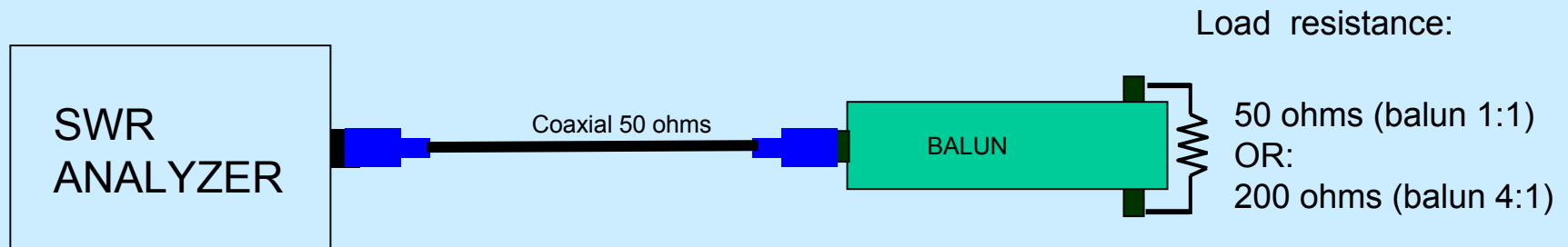
# TESTING A BALUN WITH AN SWR ANALYZER

These tests verify:


- Winding inductance
- Winding distributed capacitance



The minimum SWR should be below 1.5  
In the middle of the balun's frequency range

Indicates low losses

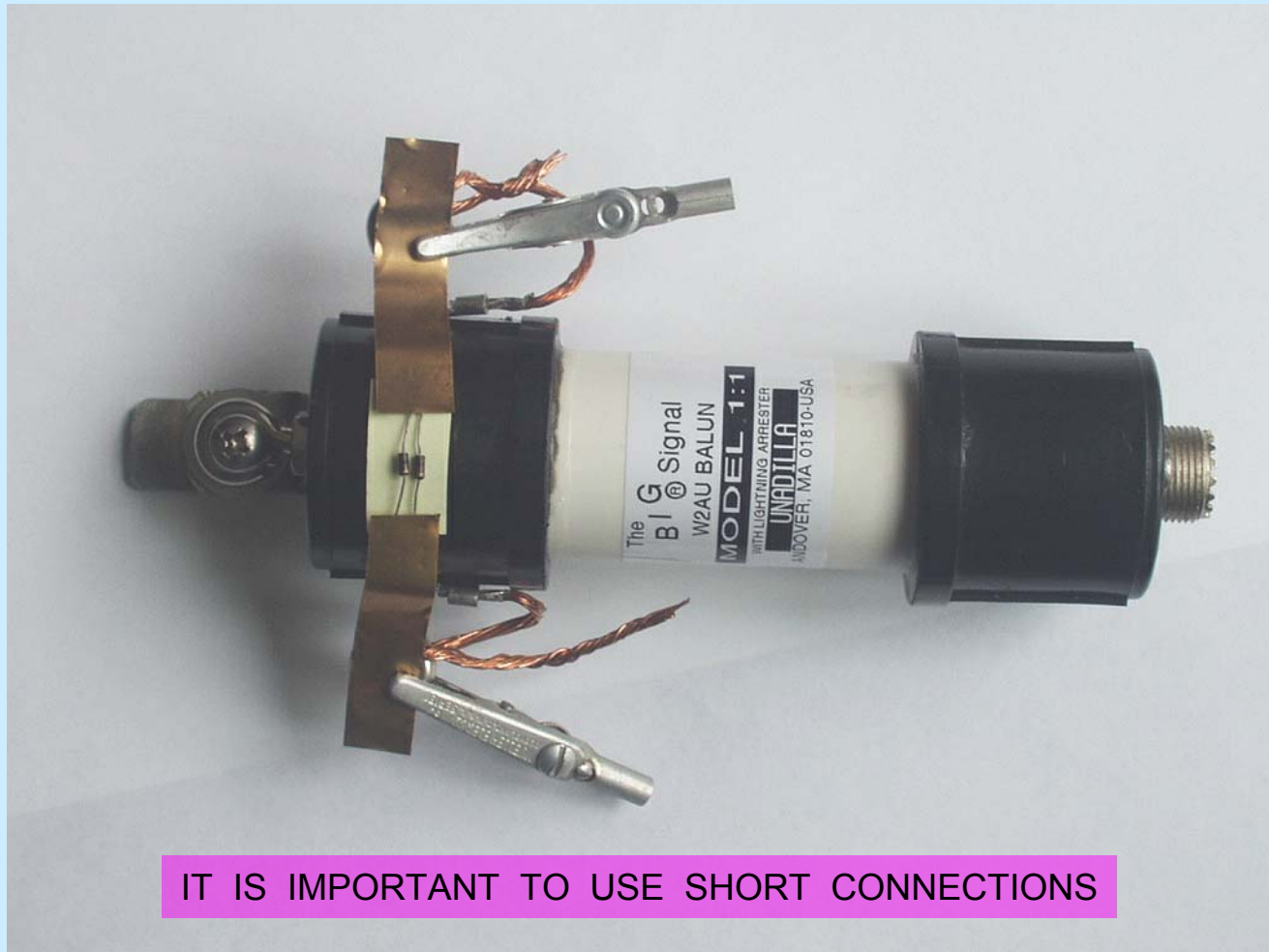
# CONNECTING THE LOAD RESISTANCE 50 Ω HERE



CH1 S11 SWR 100 m / REF 1

1: 1.4318 ← SWR

MEASURED SWR WITH A 50 ohms LOAD

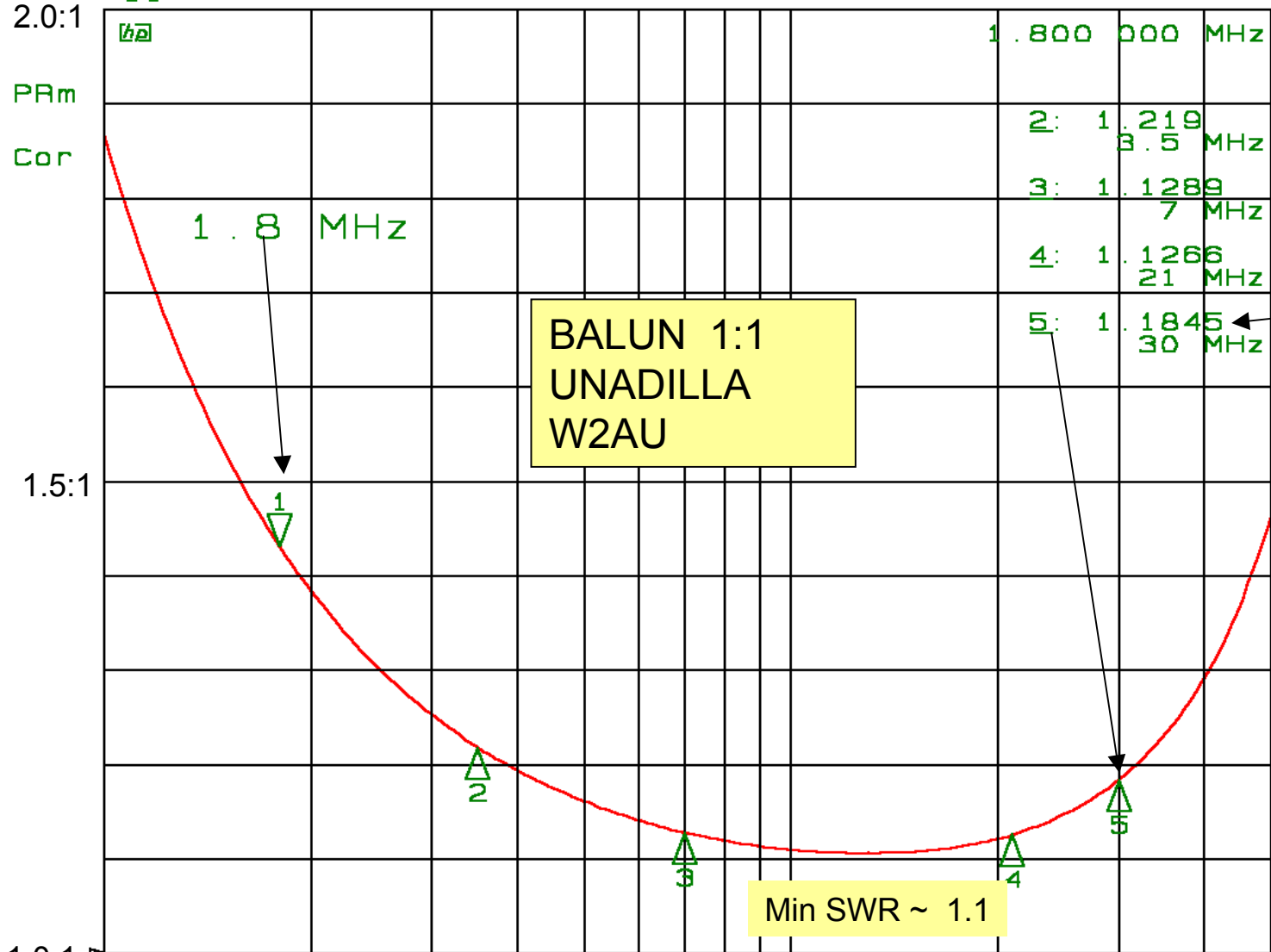

BALUN 1:1  
UNADILLA  
W2AU

Min SWR ~ 1.1

START 1.000 000 MHz STOP 50.000 000 MHz

1 MHz

10 MHz


50 MHz

CH1 S<sub>11</sub> 400 mU FS 1: 44.363 Ω 16.041 Ω 1.4183 μH  
 20 Sep 2003 21:30:28  
 1.800 000 MHz

PRm  
 Cor

SCALE  
 400 mUnits FS

2: 48.547 Ω  
 9.668 Ω  
 3.5 MHz  
 3: 50.367 Ω  
 6.0801 Ω  
 7 MHz  
 4: 55.604 Ω  
 8.164 Ω  
 21 MHz  
 5: 58.953 Ω  
 1.828 Ω  
 20 MHz

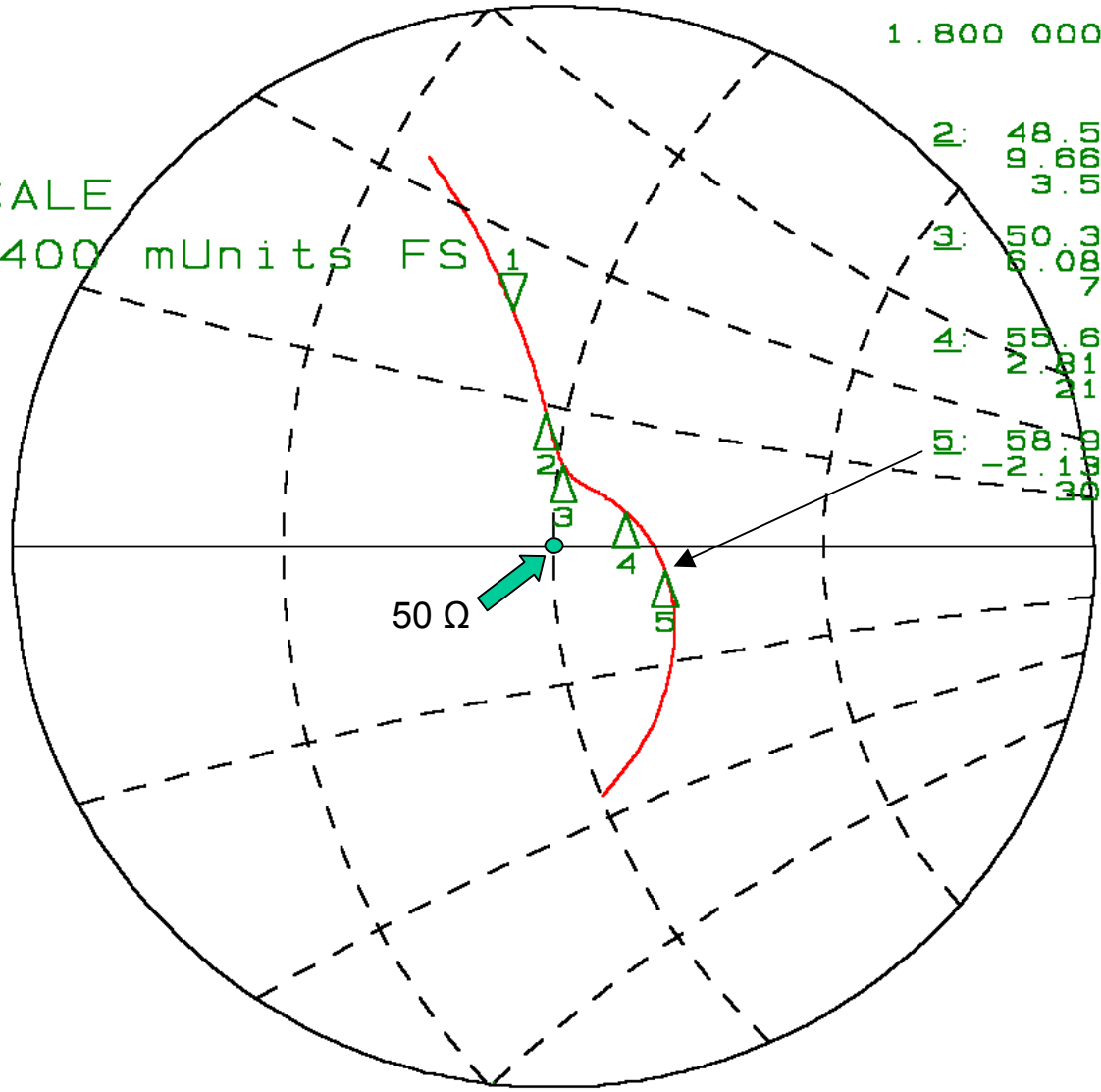


BALUN 1:1  
 UNADILLA  
 W2AU

IMPEDANCE  
 vs  
 Frequency  
 with a 50  
 ohm load


START 1.000 000 MHz STOP 50.000 000 MHz

MEASURED SWR WITH A 50 ohms LOAD

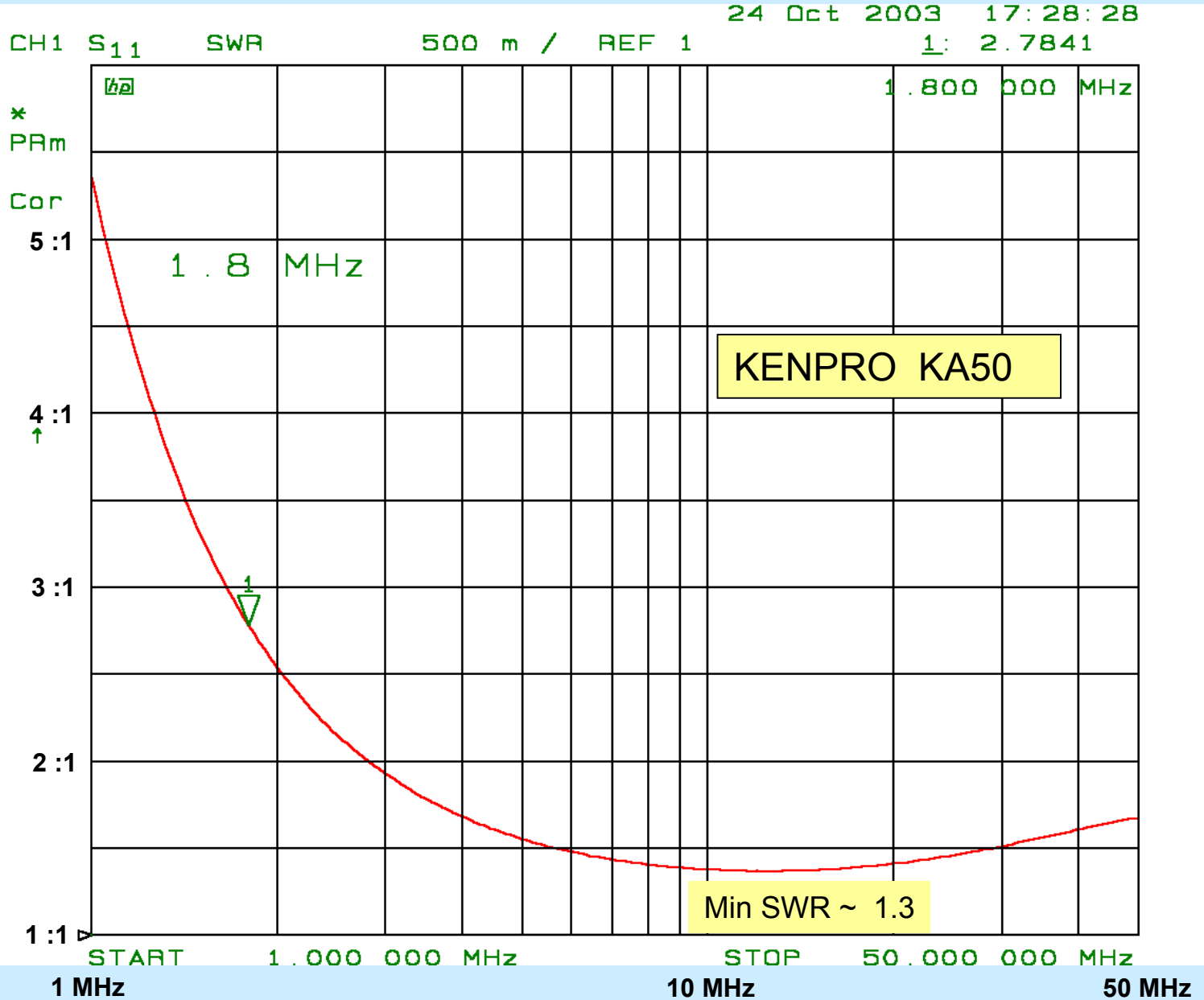

CH1 S<sub>11</sub> SWR 500 m / REF 1 4: 1.2785



MEASURED SWR WITH A 200 ohms LOAD

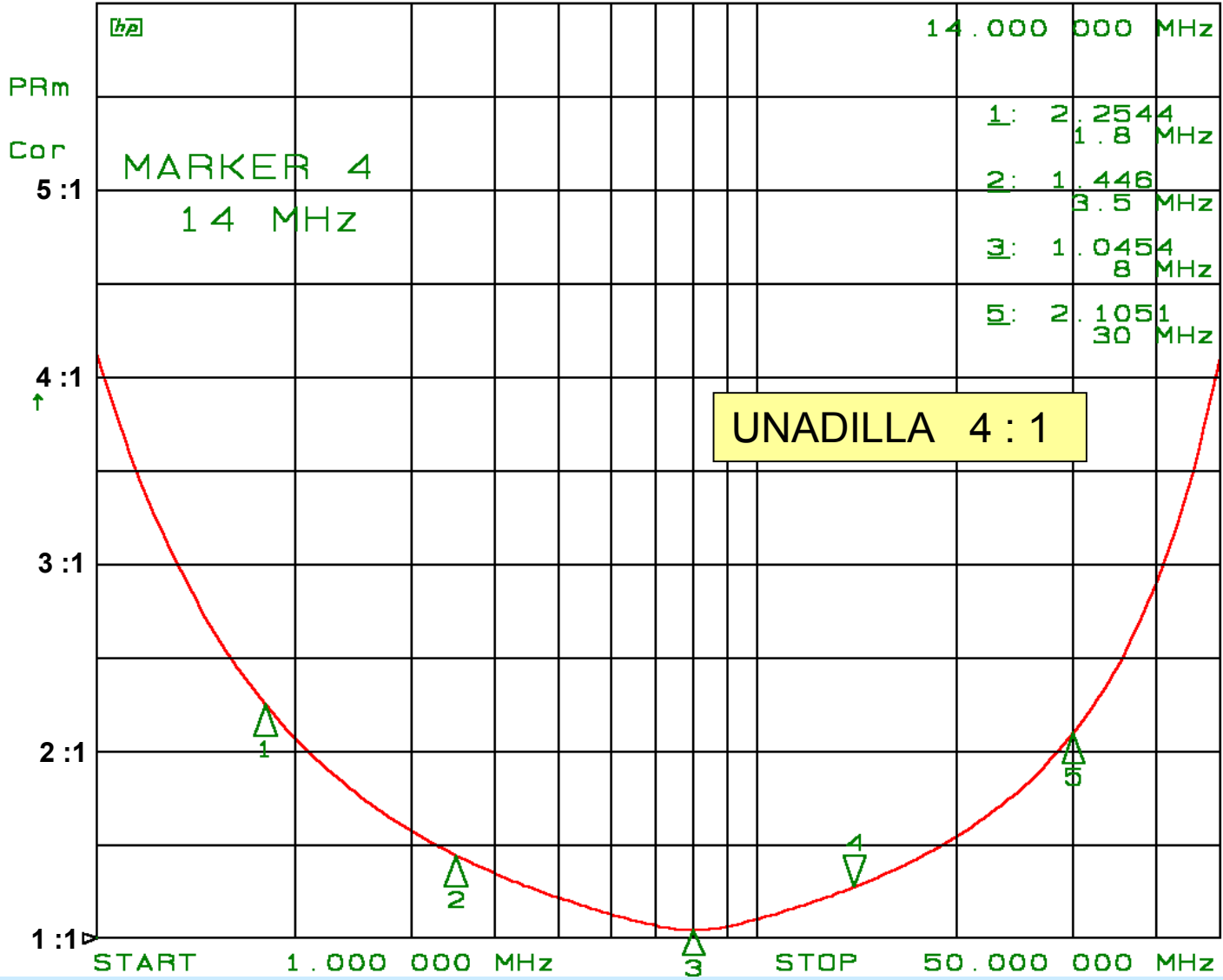
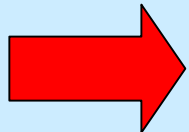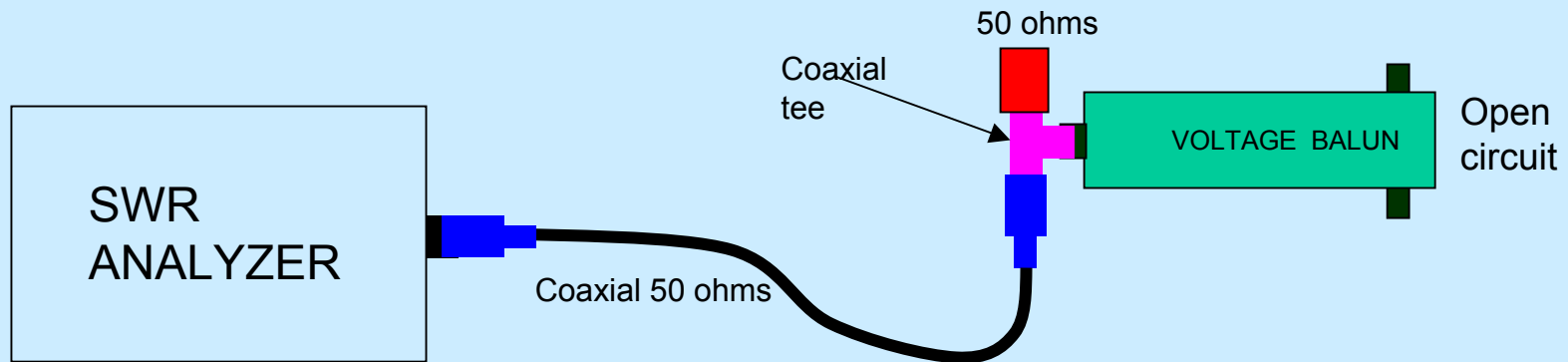
# OPEN CIRCUIT TESTS WITH THE SWR ANALYZER

These tests verify:

- Winding inductance
- Winding distributed capacitance
- Quality of the winding insulation




The minimum SWR should be below 1.1  
in the middle of the balun's frequency range

Indicates low losses


# OPEN CIRCUIT TESTS WITH THE SWR ANALYZER

23 Sep 2003 11:17:02

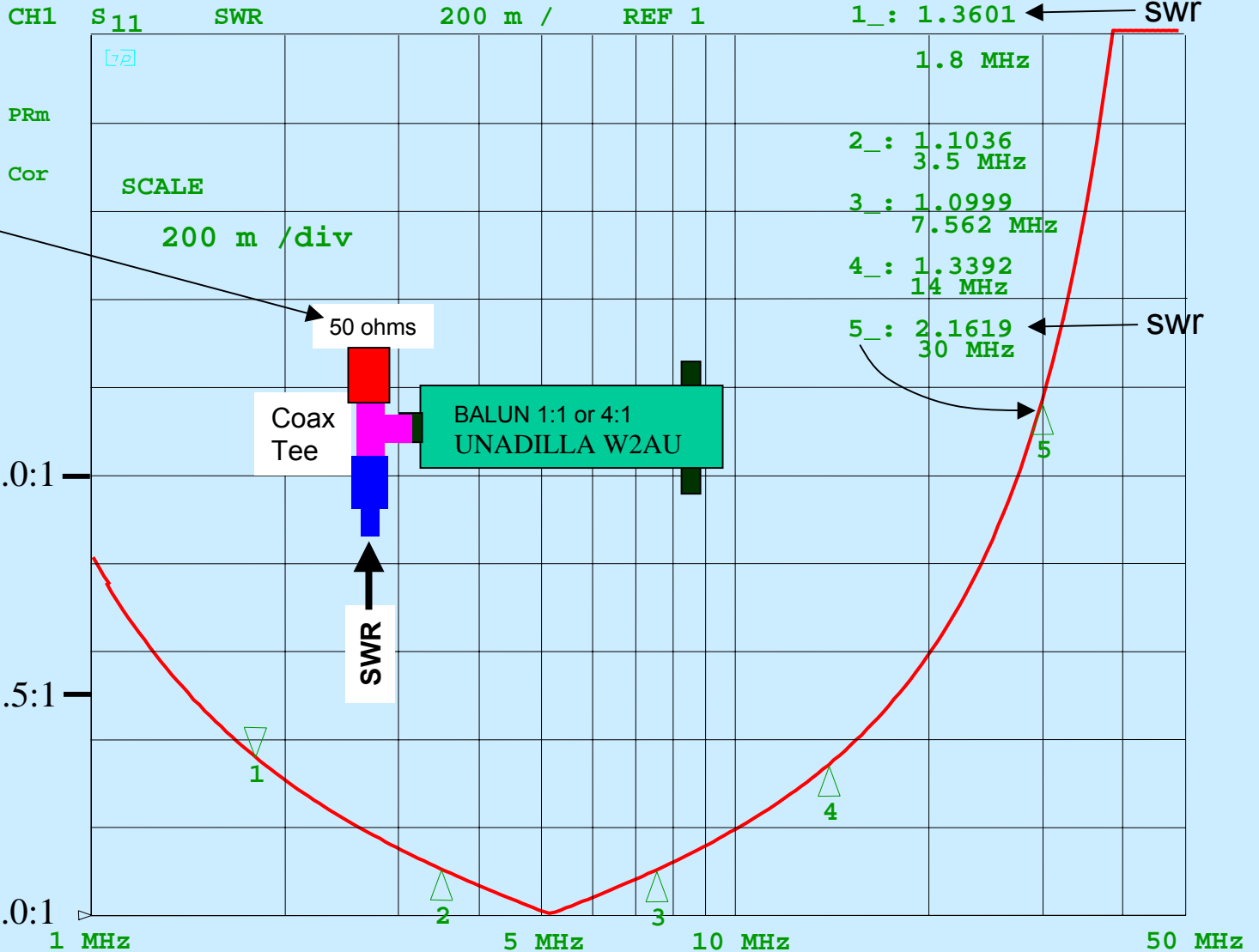

Always 50Ω  
whatever  
the Z ratio

# OPEN CIRCUIT TESTS WITH A VNA

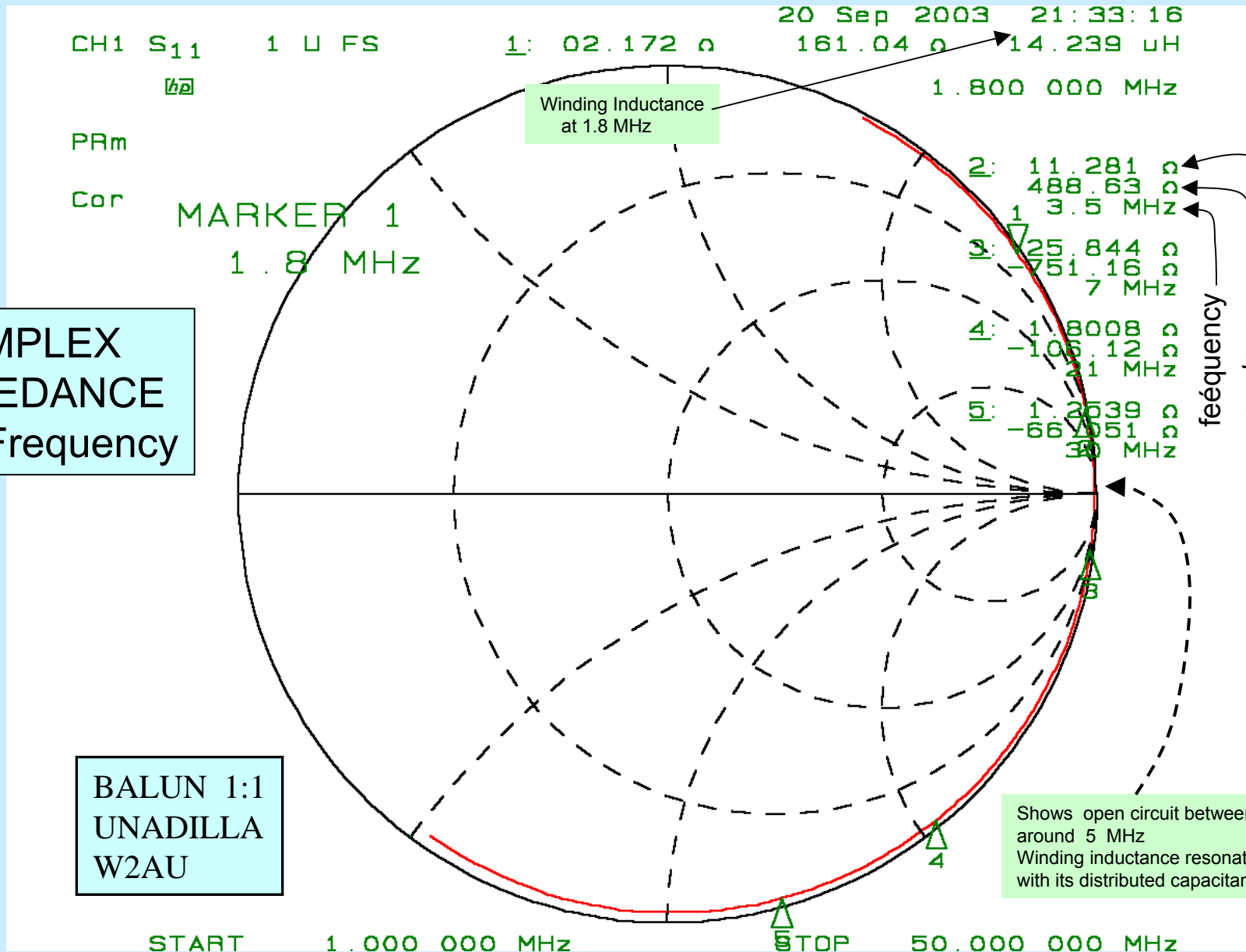

COMPLEX IMPEDANCE vs Frequency

BALUN 1:1 UNADILLA W2AU

# CURRENT BALUNS

QUESTION: How many independent conductors at RF frequencies do we have in a coaxial cable ? 1, 2, 3 or 4 conductors ?

There are 3 independent conductors:

- The center conductor
- The inner surface of the shield
- The outer surface of the shield



Note that the RF current that flows on the outer surface of the shield is independent of the inner shield current.

This is so because at RF frequencies, the current penetrates very little inside the conductors. This is called SKIN EFFECT.


Note also that the SWR only applies to the inner shield currents (and center cond).  
The SWR is basically independent of the outer shield currents.

## SHIELDED LOAD

With a shielded load, the current stays inside the coax

There is no current on the outside of the coax, whatever the load (open, short or terminated)

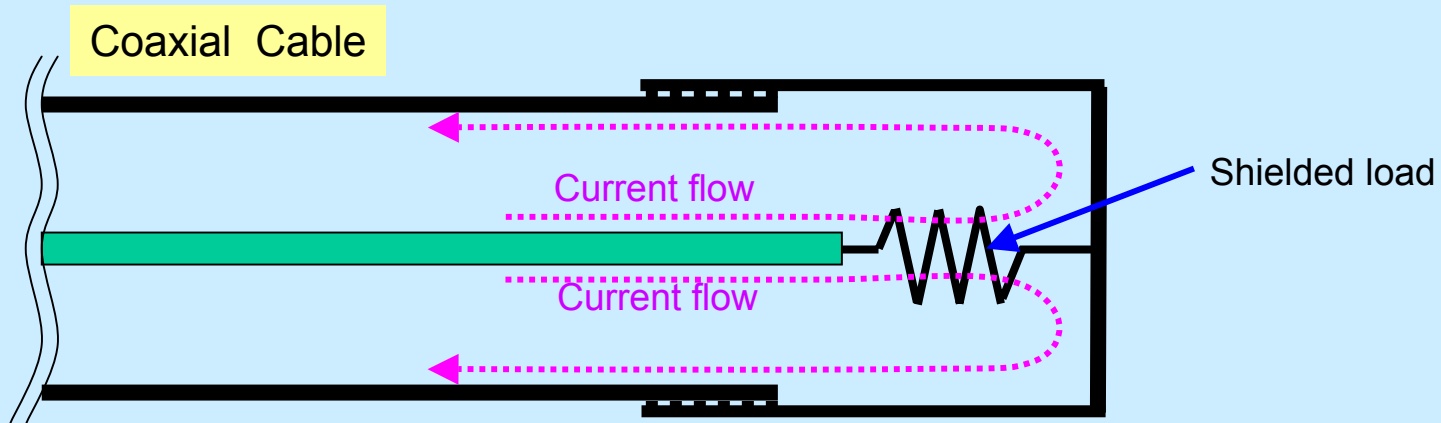Adding ferrites on the outside of the coax has NO effect, since no current flows on the outside of the shield.




## UNSHIELDED LOAD

A dipole is an unshielded load

An unshielded load causes current to flow on the outer surface of the coax, since it picks up radiated currents. In fact it is part of the antenna. The radiation pattern changes.

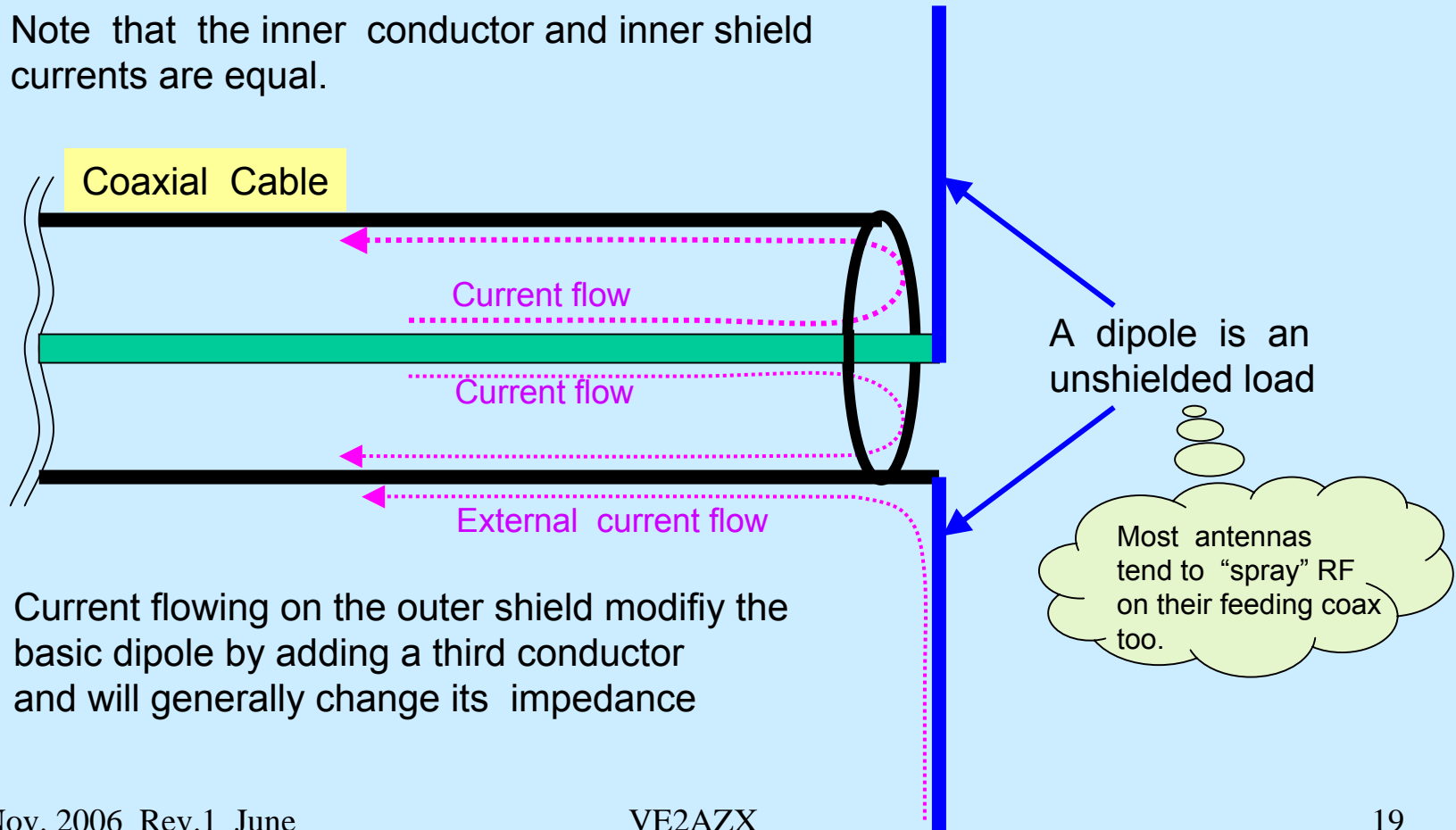Note that the inner conductor and inner shield currents are equal.




## UNSHIELDED LOAD

Adding a ferrite core adds resistance (at RF) only on the OUTSIDE of the coax.

The ferrite core reduces the shield currents

The ferrite core has NO effect on the internal coax currents, besides restoring the dipole impedance and normal radiation pattern.

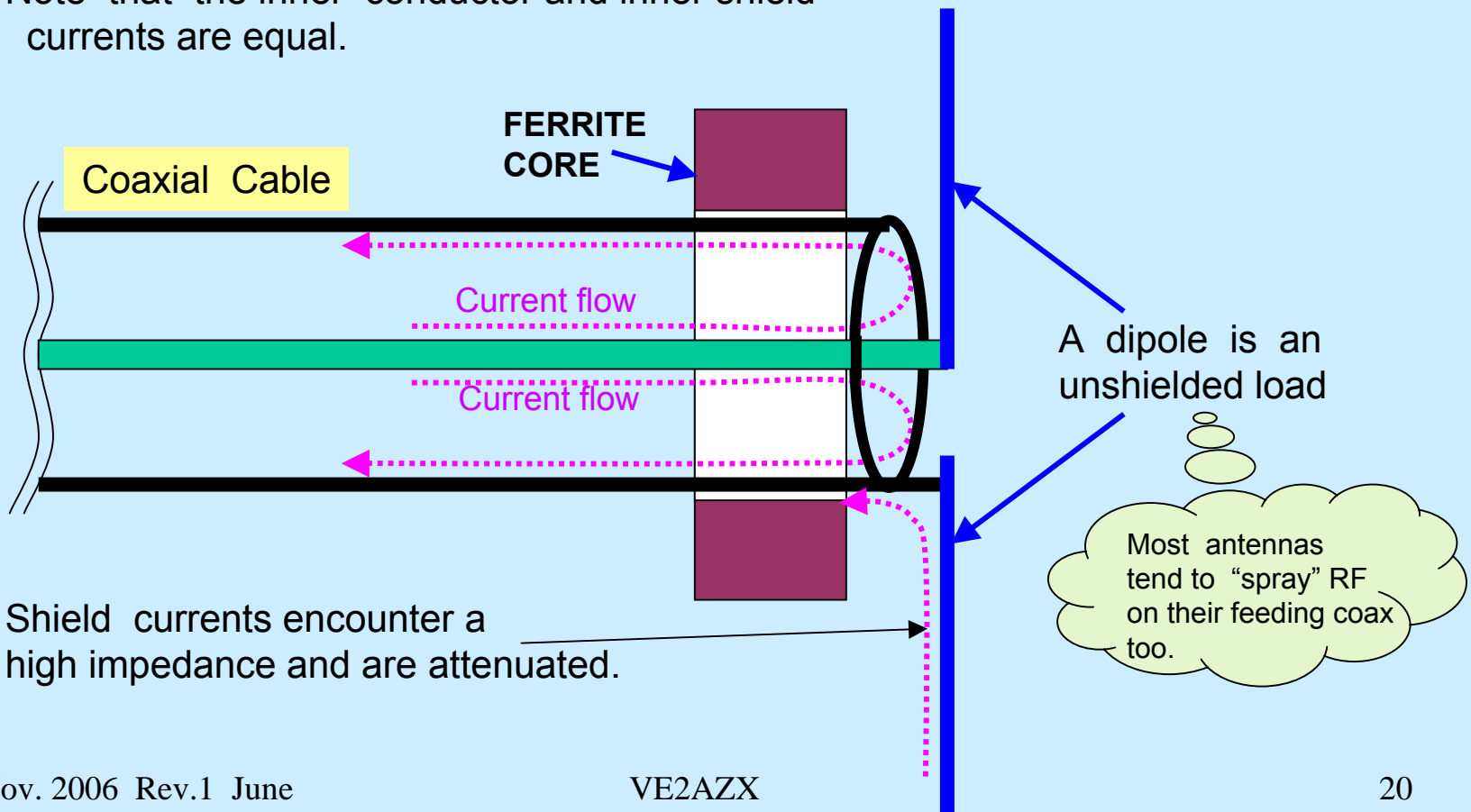
Note that the inner conductor and inner shield currents are equal.


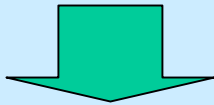
# CURRENT BALUNS



How much Resistance is Required when Feeding a dipole with a coaxial cable ?

A coax cable feeds a dipole at its center, or with an offset



Equivalent Circuit  
**The coax is part of the antenna**


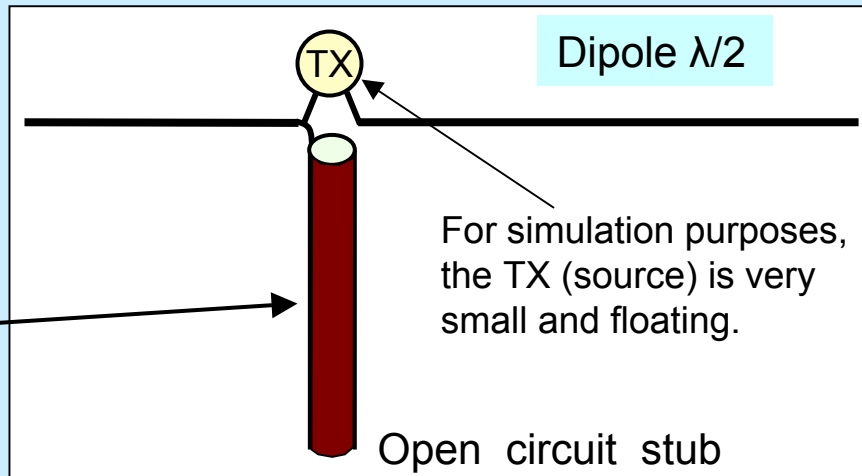
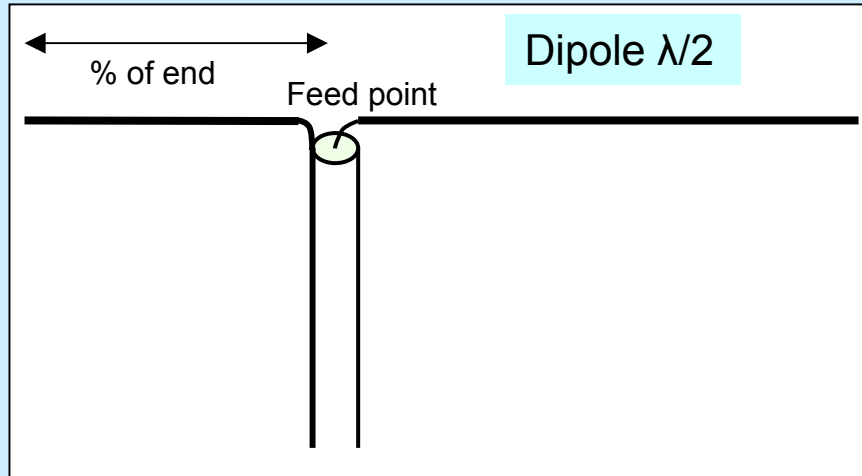
$\lambda/4$  open stub  
Is the **WORST** length – since it reflects a short


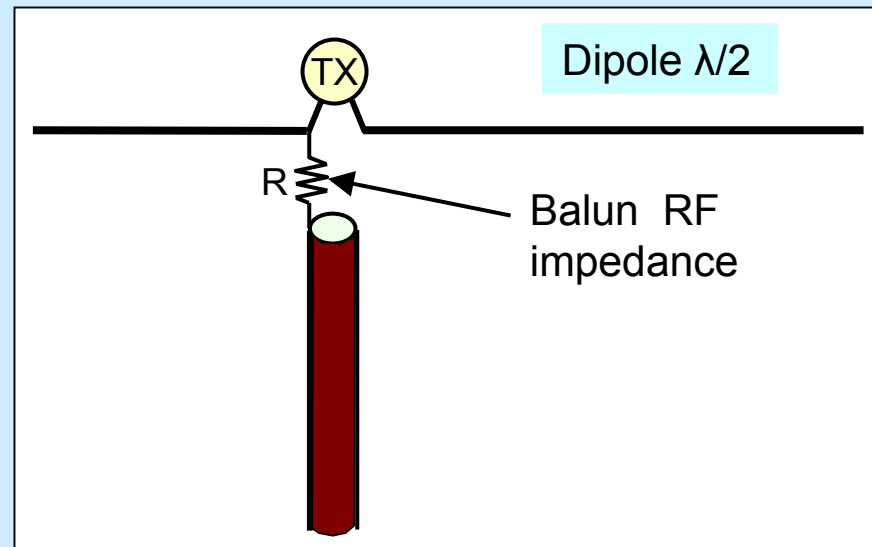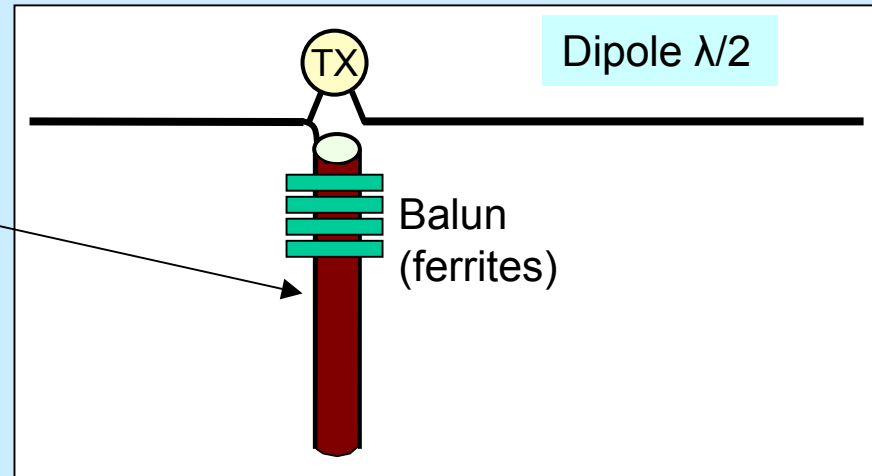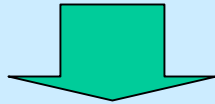
# CURRENT BALUNS

Feeding a dipole with a coaxial cable

To decrease the stub current:  
A current balun is inserted.  
It adds a series impedance  
on the outside of the coax.






Balun Equivalent Circuit

What is the minimum value of  
Impedance that I can have ...


That will have little effect on  
the gain and impedance of  
the dipole antenna ?

# CURRENT BALUNS

Feeding a dipole with a coaxial cable

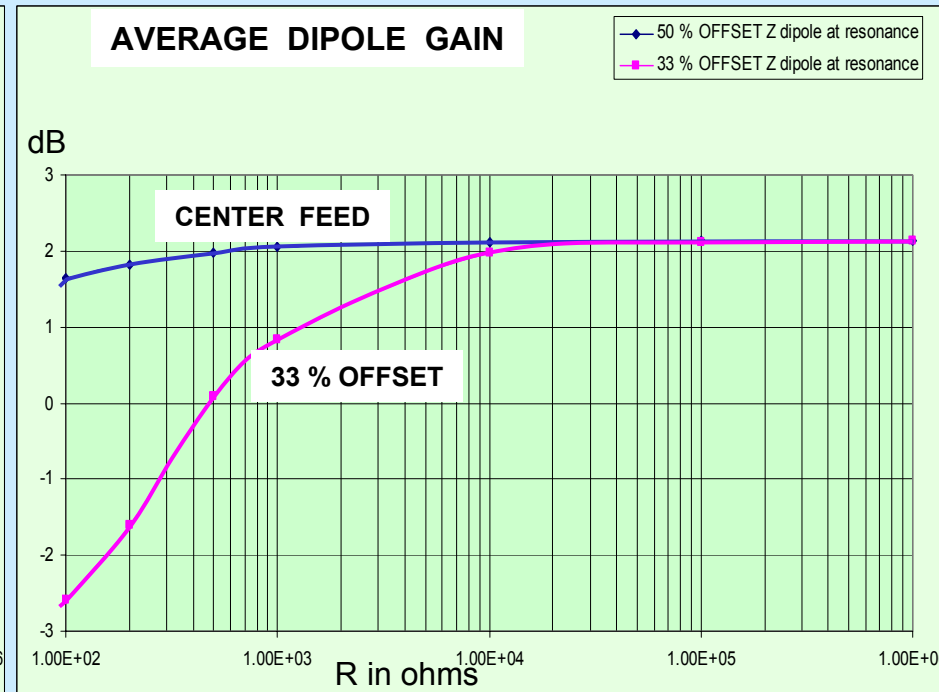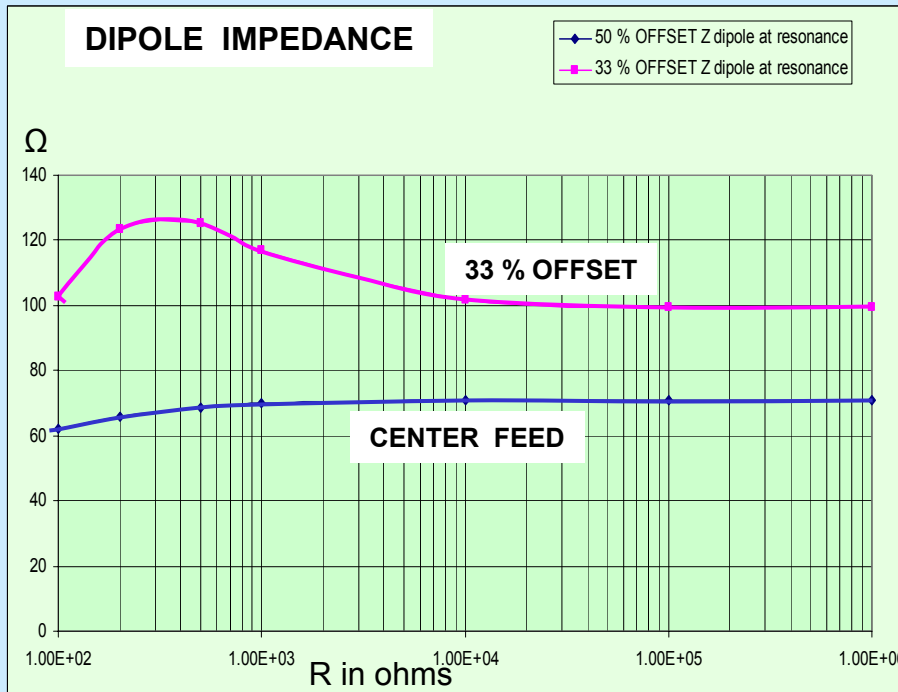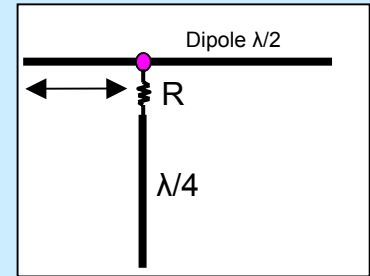


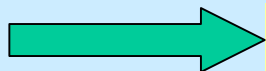
If feeding at the center (50%):  $R > 1000$  ohms  
 If feeding at 33% from end:  $R > 10000$  ohms



It's easier to feed at the center

# CURRENT BALUNS

## 1:1 CURRENT BALUN

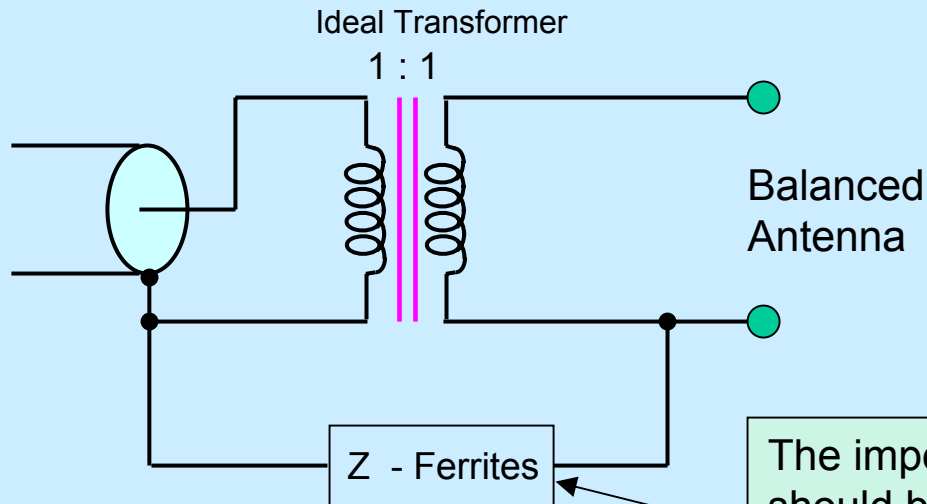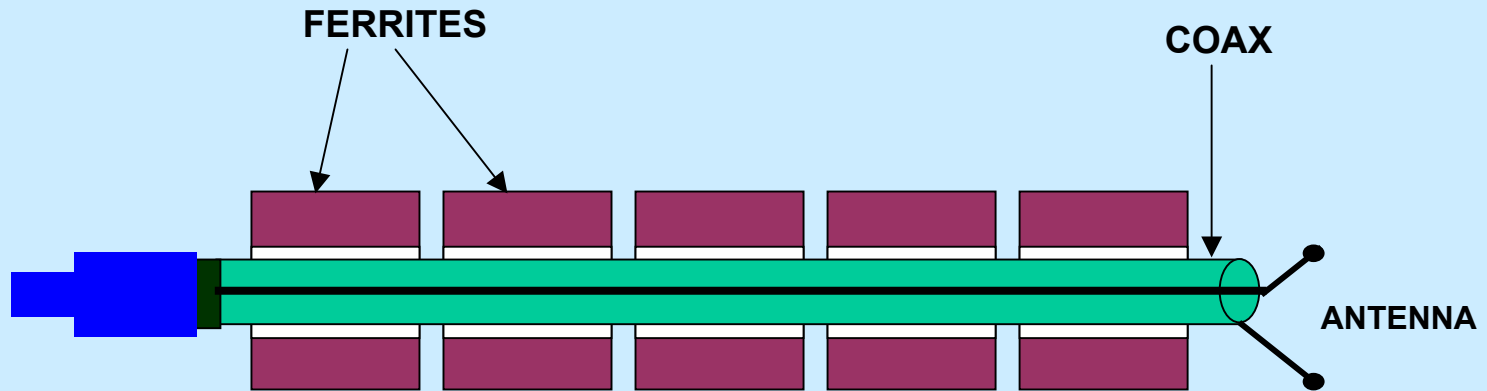

Equivalent  
Circuit at RF

Nov. 2006 Rev.1 June  
2008

VE2AZX

The impedance of the ferrites  
should be high (> 1000 ohms)  
for a well balanced output 24

# FERRITE IMPEDANCE


## DEPENDS ON...

- MATERIAL
- LENGTH
- VOLUME OF MATERIAL
- VARIES WITH FREQUENCY
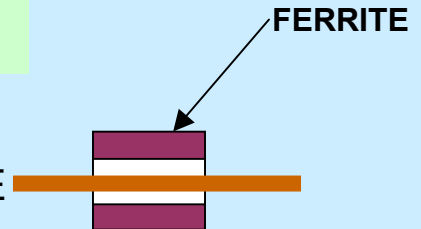
## - TO CALCULATE THE IMPEDANCE Z: (approx.)

IMPEDANCE OF ONE TURN FOR ONE FERRITE  
multiplied by...  
NUMBER OF FERRITES  
multiplied by ...  
(NUMBER OF TURNS) squared

- NOTE: 1 TURN = FERRITE ON A STRAIGHT WIRE



## FERRITE IMPEDANCE


### - FERRITES VS IRON POWDER ... TWO DIFFERENT MATERIALS

- **FERRITE**: HAS A HIGH PERMEABILITY (10 to 15000)  
GIVING A HIGH INDUCTANCE FOR A SMALL NUMBER OF TURNS  
  
BUT THE INDUCTANCE OBTAINED IS NOT STABLE AND Q FACTOR IS LOW  
  
OK FOR TRANSFORMERS AND BALUNS
- **IRON POWDER**: LOWER PERMEABILITY ... LOWER INDUCTANCE,  
GIVES A STABLE, HIGH Q INDUCTANCE (EX.: VFO, FILTERS, TUNERS)
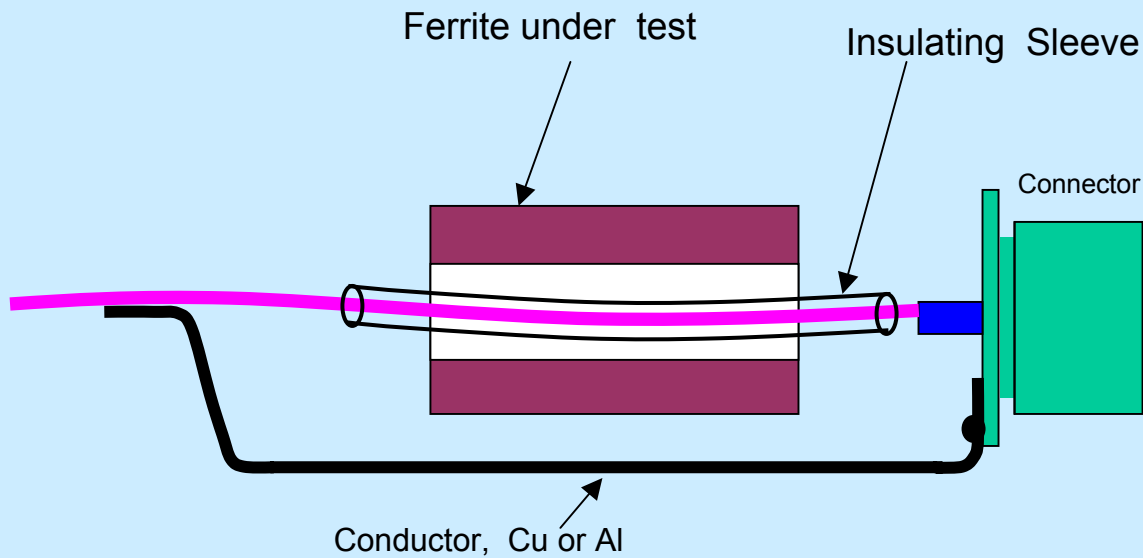
# MEASUREMENT OF FERRITE IMPEDANCE

USING AN SWR ANALYZER OR A VECTOR NETWORK ANALYZER

Allow measuring separately the Resistive and Inductive Components




SWR ANALYZER  
With IMPEDANCE CAPABILITY  
- OR -  
VECTOR NETWORK  
ANALYZER



# IMPEDANCE MEASUREMENTS



CLAMP ON FERRITE  
FOR RG-8


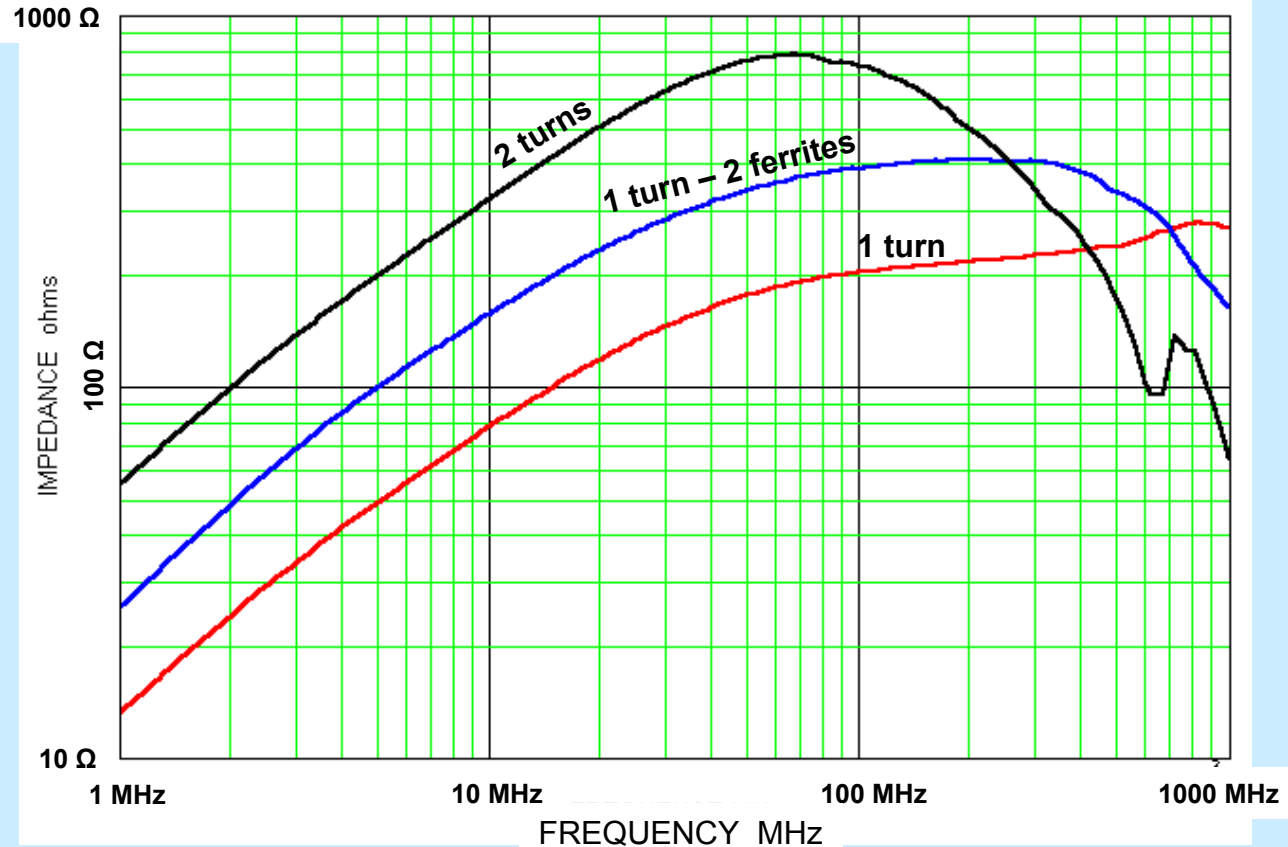


**YIELDS 80 ohms at 10 MHz for 1 turn**

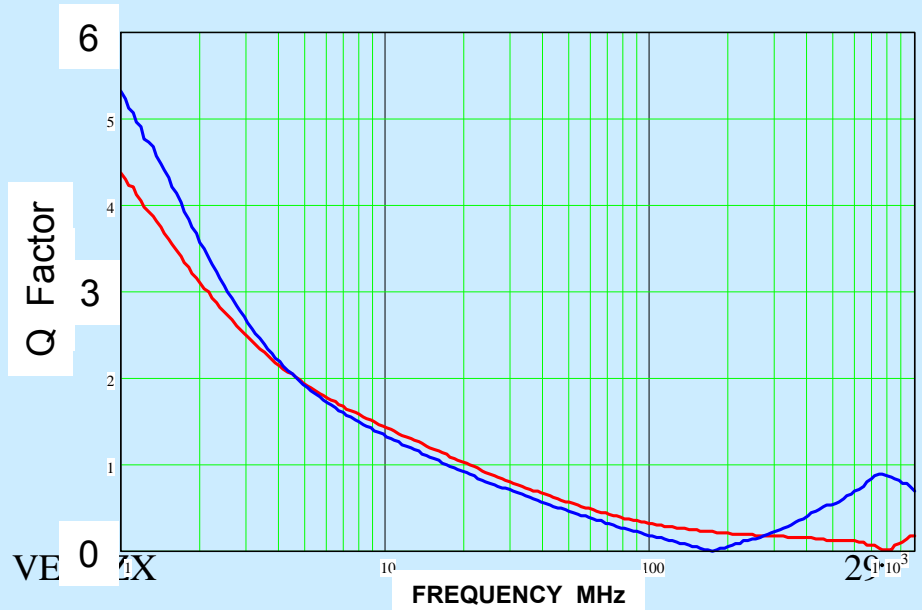
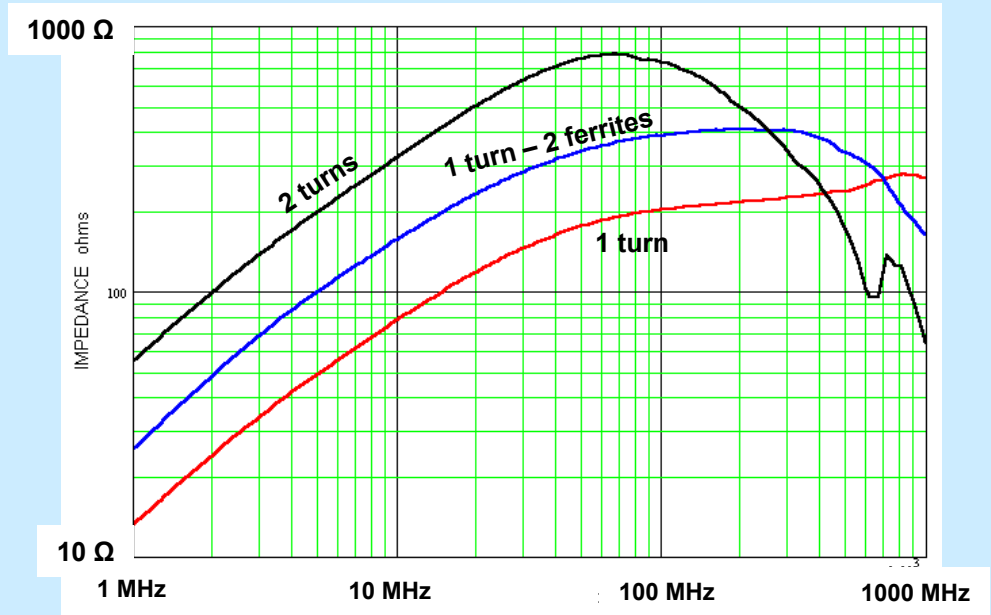
# IMPEDANCE MEASUREMENTS



- ABOVE 20 MHz THE Q FACTOR < 1  
THE IMPEDANCE BECOMES RESISTIVE




# IMPEDANCE MEASUREMENTS

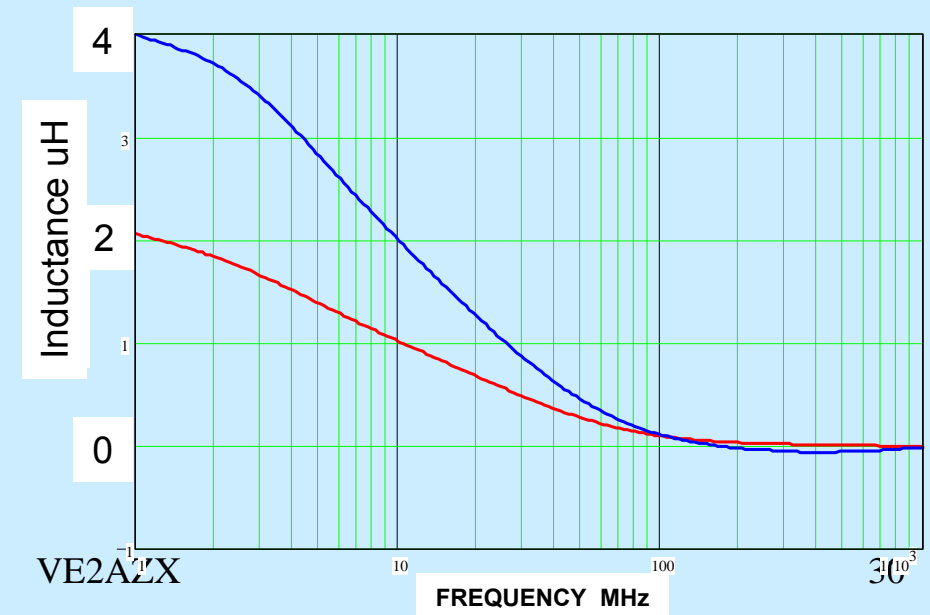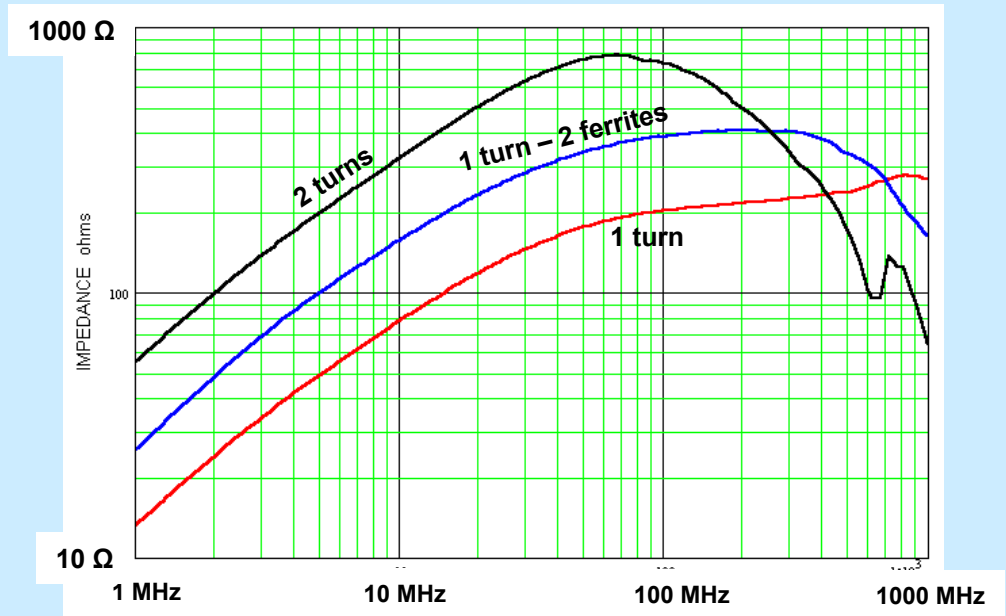


- THE INDUCTANCE DECREASES AS THE FREQUENCY IS INCREASED
- THE INDUCTANCE DISAPPEARS WHEN  $F > 100$  MHz

# IMPEDANCE MEASUREMENTS

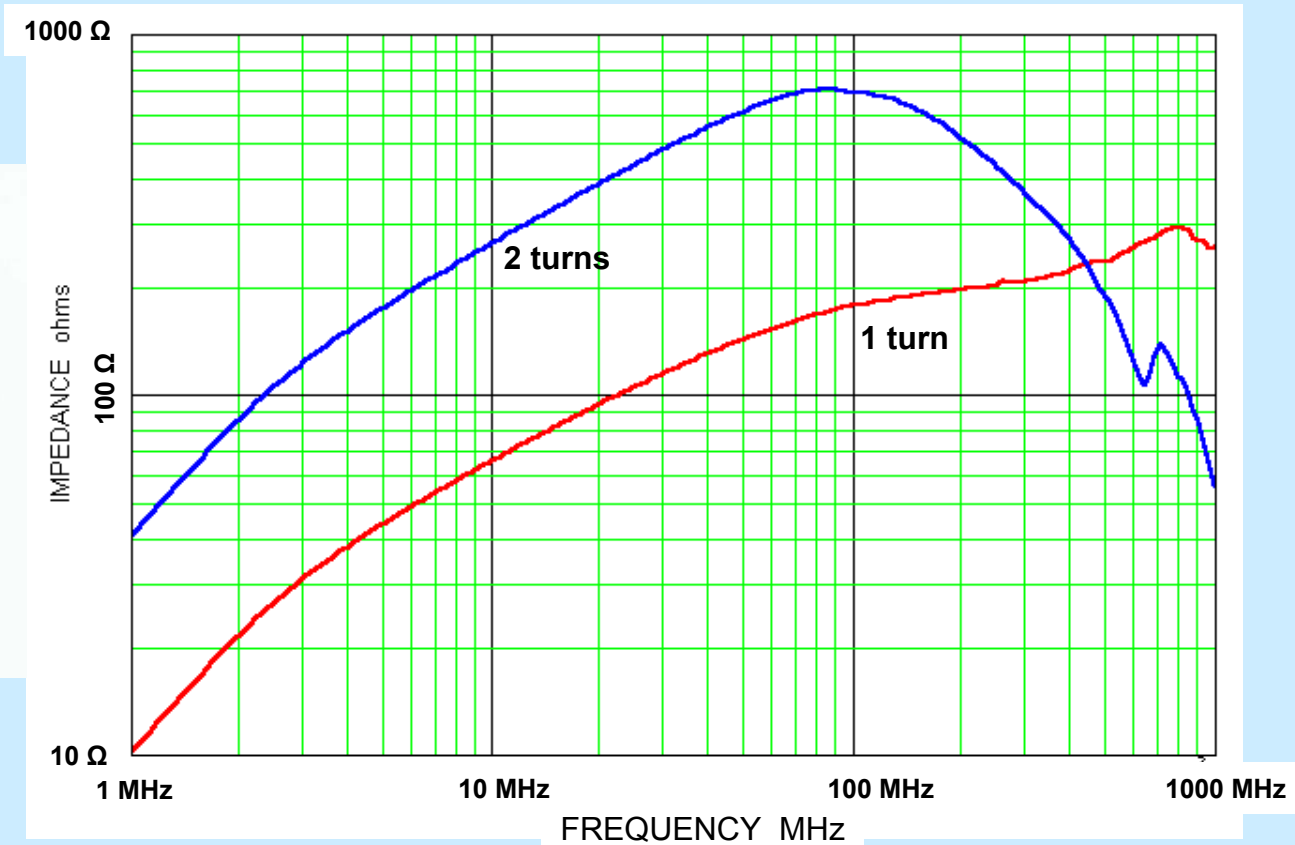

- THIS IMPEDANCE CURVE IS SIMILAR TO THE PREVIOUS CORE

# IMPEDANCE MEASUREMENTS

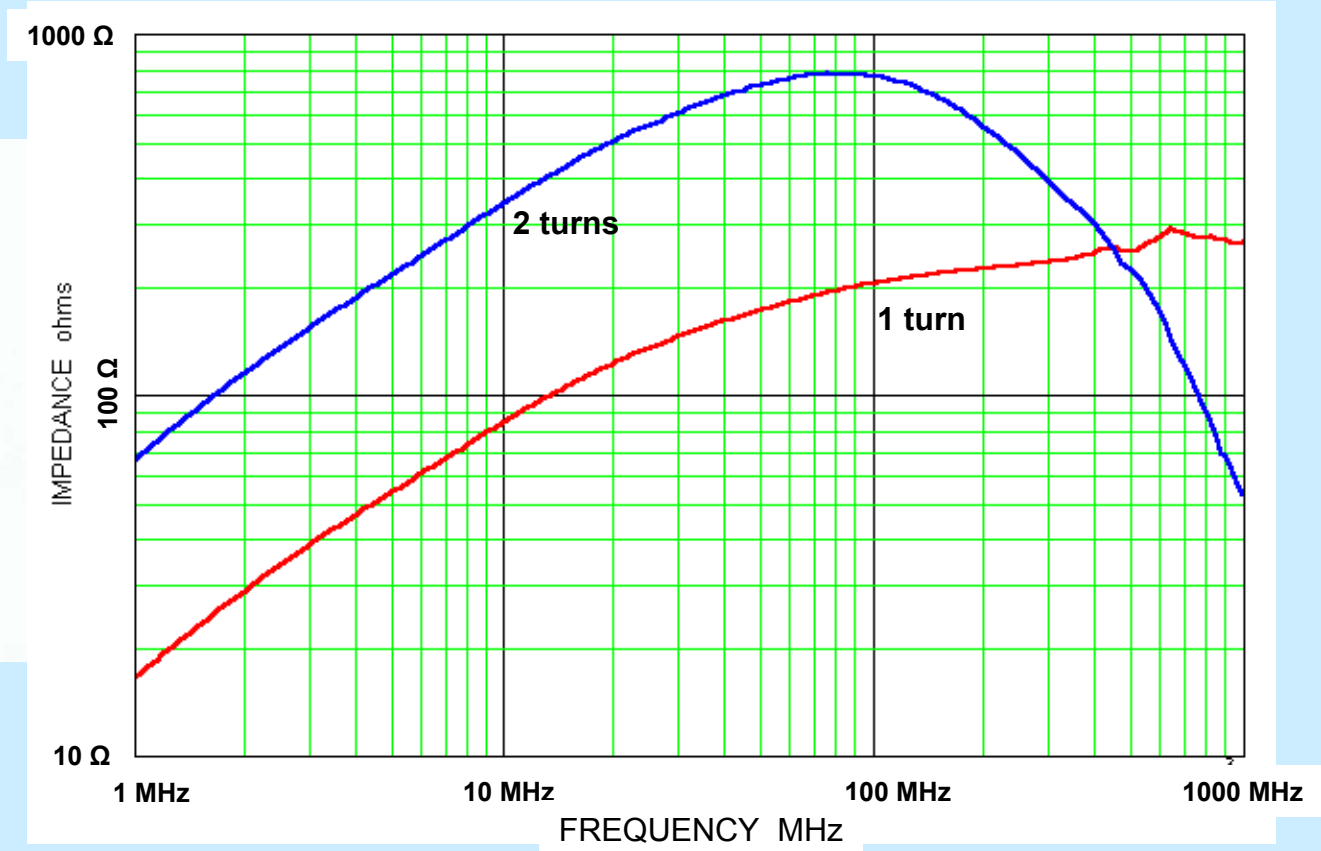


- THIS IMPEDANCE CURVE IS SIMILAR TO THE PREVIOUS CORE

# IMPEDANCE MEASUREMENTS



RECTANGULAR  
CLAMP-ON FERRITE


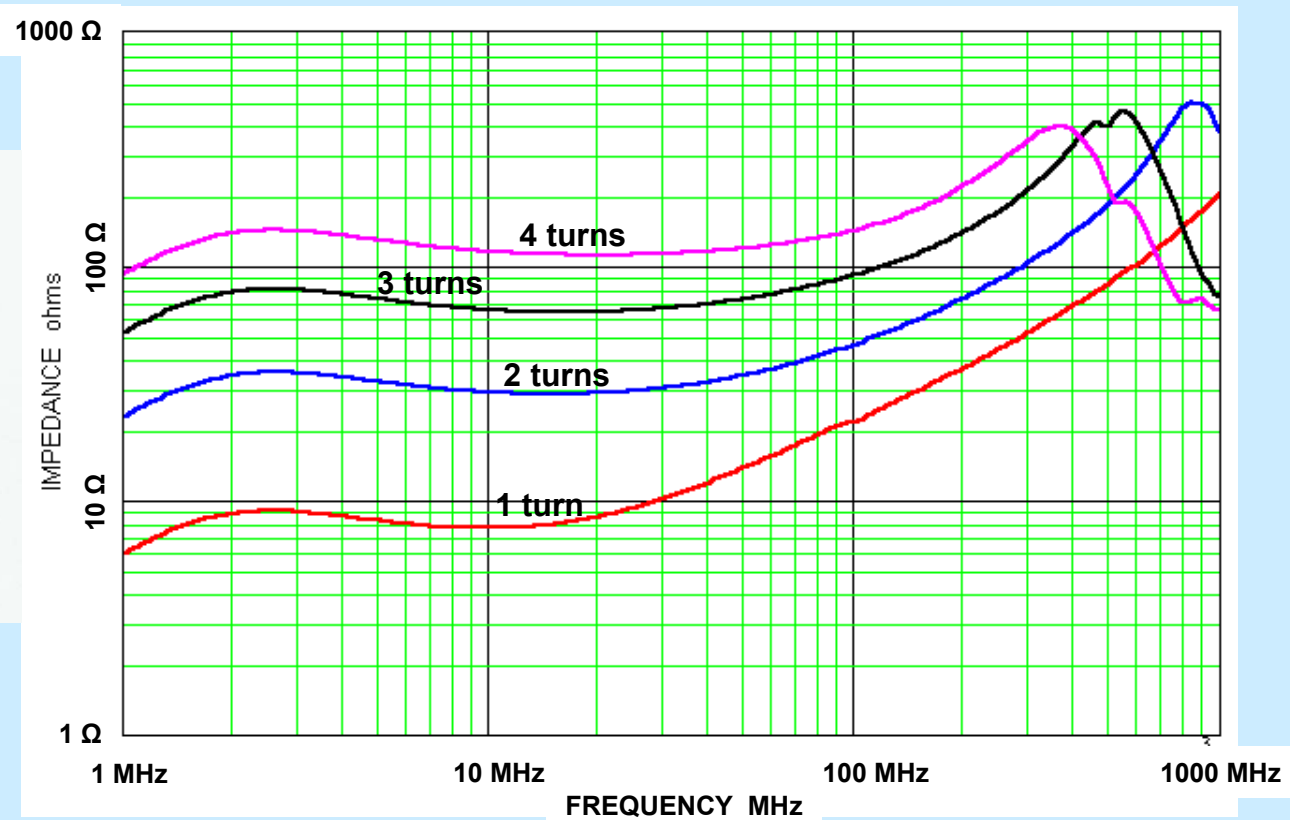


- GIVES ~ 10% IMPEDANCE OF PREVIOUS CORES (8 ohms at 10 MHz for 1 turn)
- COVERS MUCH WIDER FREQUENCY RANGE
- SHOULD USE MANY TURNS: 10 TURNS GIVE 800 ohms AT 10 MHz

# IMPEDANCE MEASUREMENTS



RECTANGULAR  
CLAMP-ON FERRITE

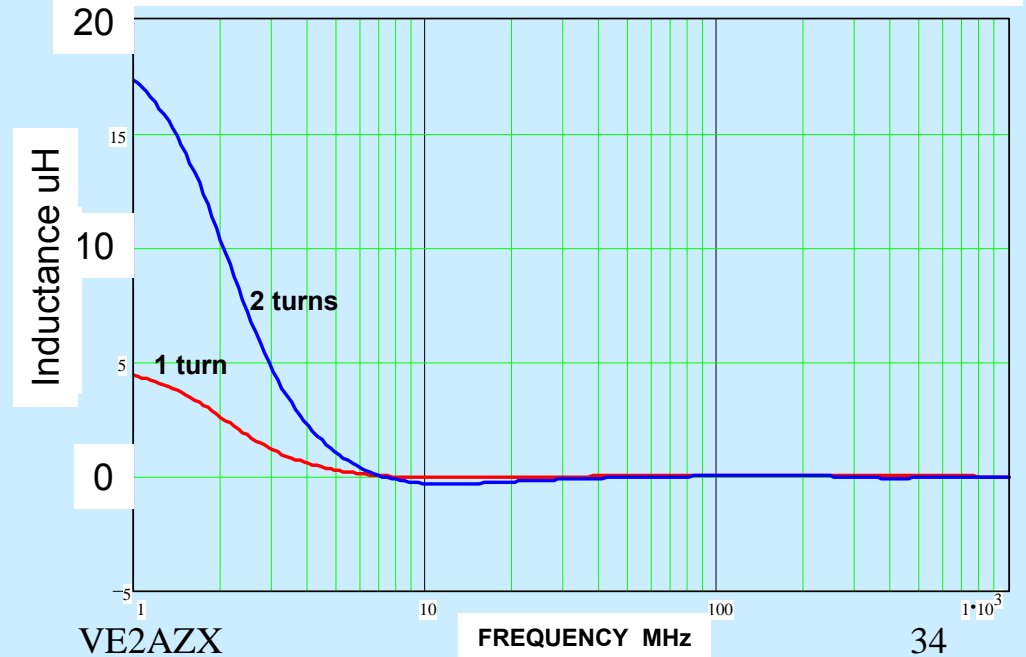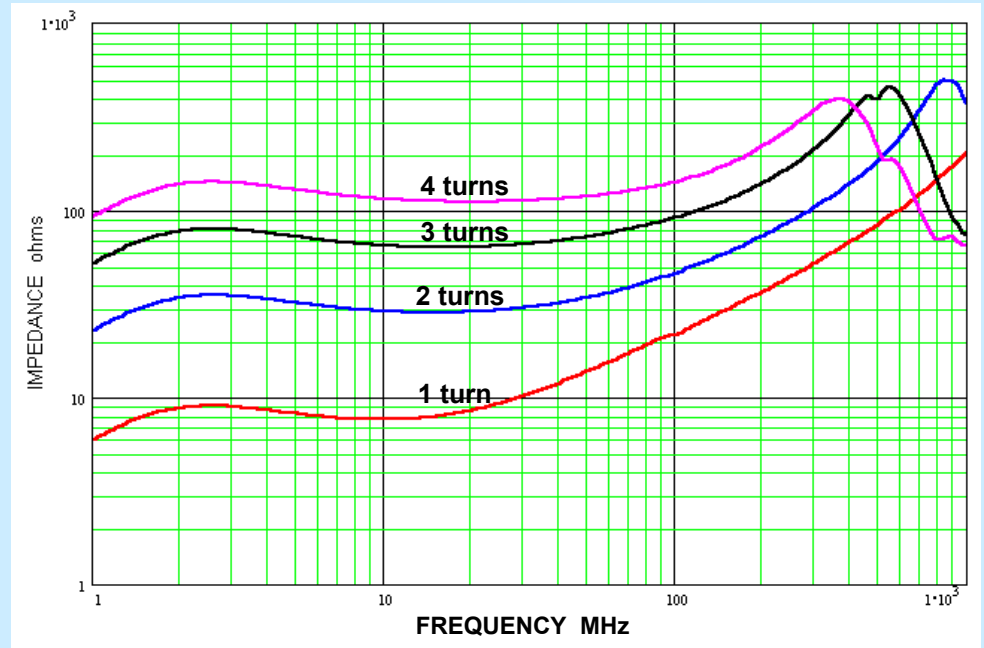


- THE INDUCTANCE DISAPPEARS  
ABOVE 6 MHz

# IMPEDANCE MEASUREMENTS




STACKED  
RECTANGULAR  
CLAMP-ON FERRITE

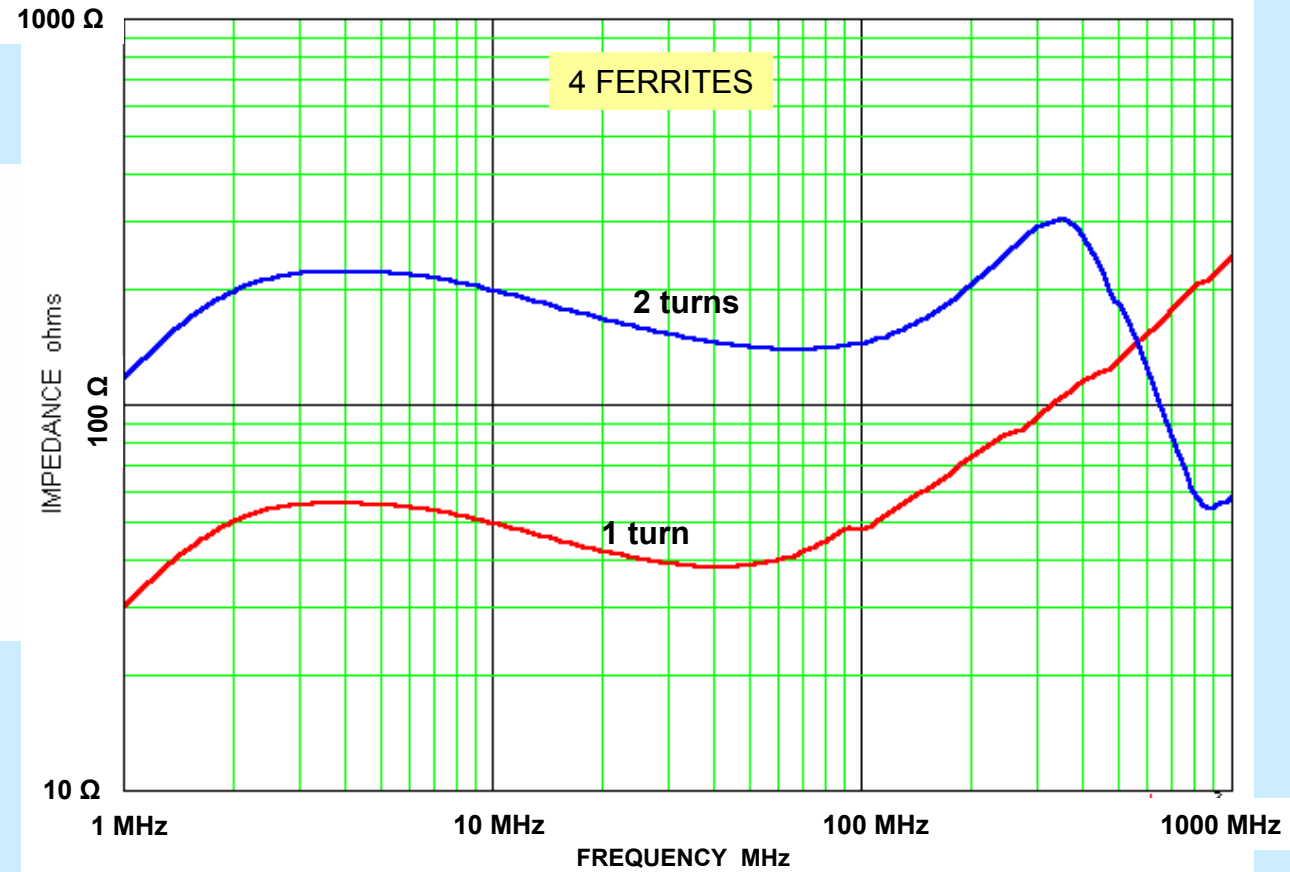


**4 TURNS WILL YIELD ~ 800 ohms**

# TESTING A FERRITE BEAD

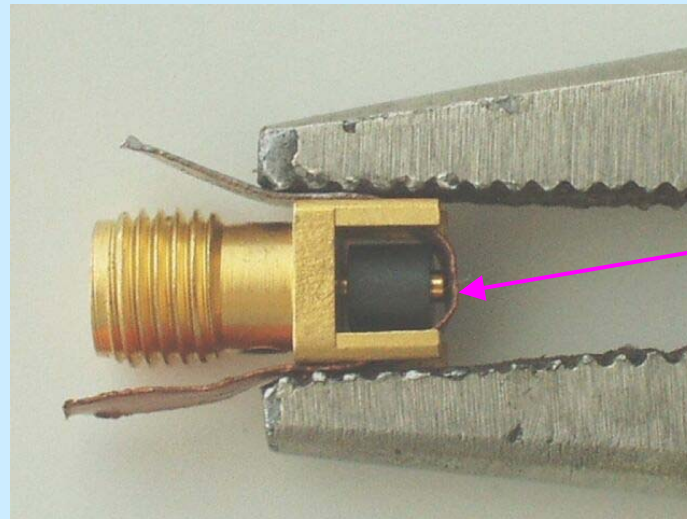


FERRITE BEAD  
APPROX. 0.1 PO. LONG.

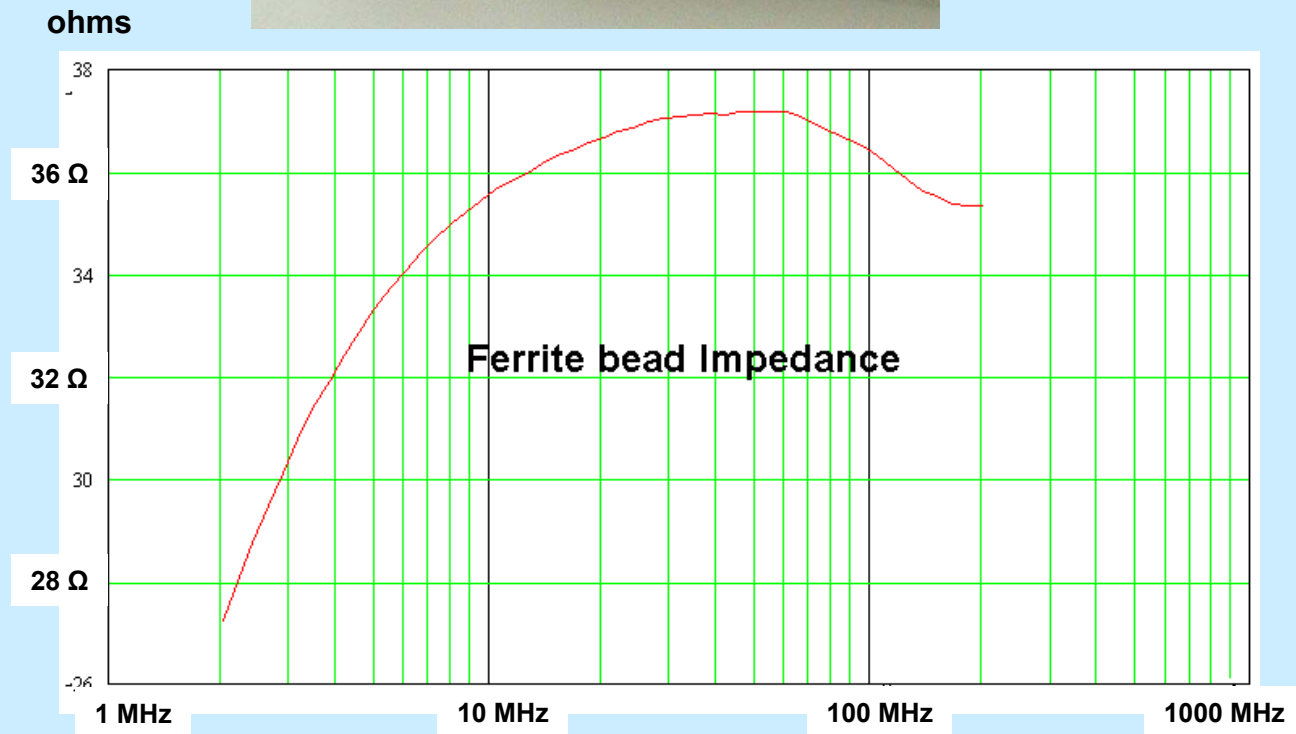

# IMPEDANCE MEASUREMENTS
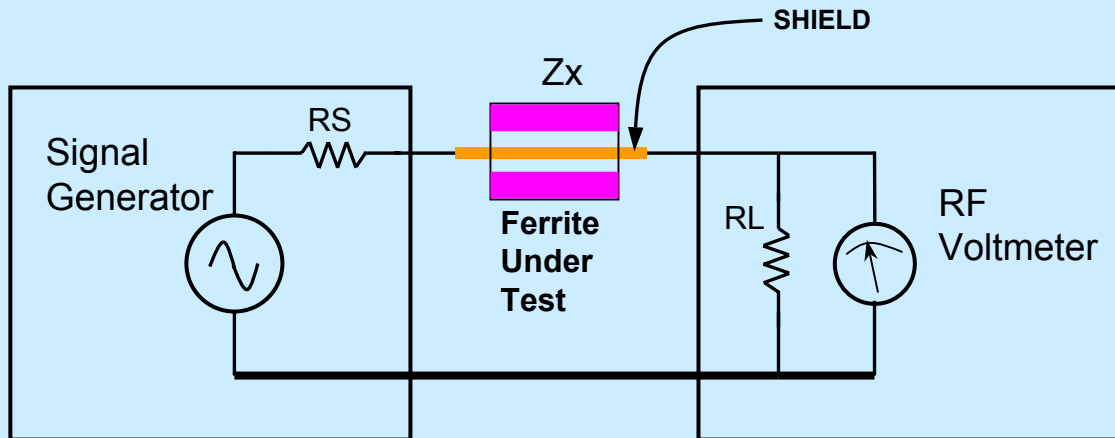
## FREQUENCY RESPONSE MODE

- Does NOT allow measuring separately the Resistive and Inductive components
- Ease of sweeping the frequency
- Reference level = 0 dB = short in place of ferrite



RS and RL are generally 50 ohms

**To calculate Zx from attenuation readings in + dB's:**  
(assumes that Zx is resistive)


$$Z_x = (R_L + R_S) \cdot (10^{\left[\frac{\text{dB}}{20}\right]} - 1)$$

# IMPEDANCE MEASUREMENTS

(Done in frequency response mode)



6 toroids 4 turns

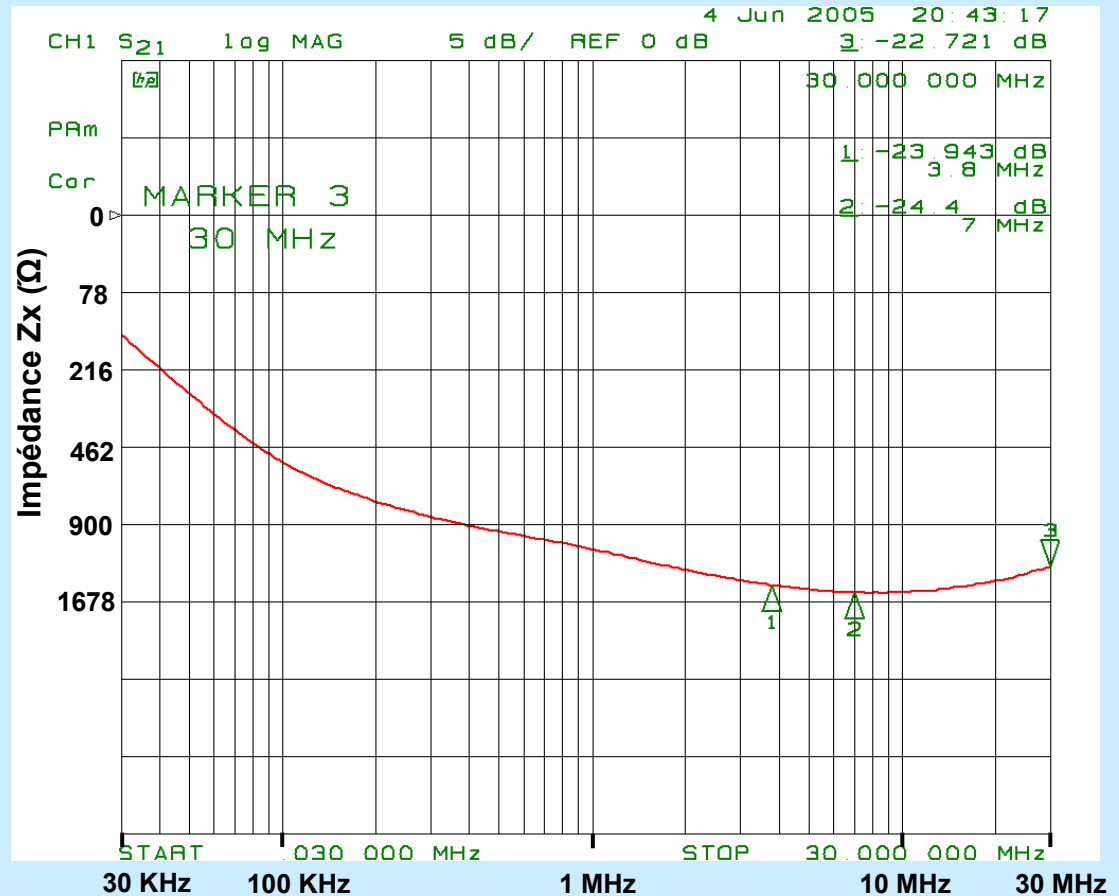


# IMPEDANCE MEASUREMENTS

(Done in frequency response mode)



6 toroids 6 turns

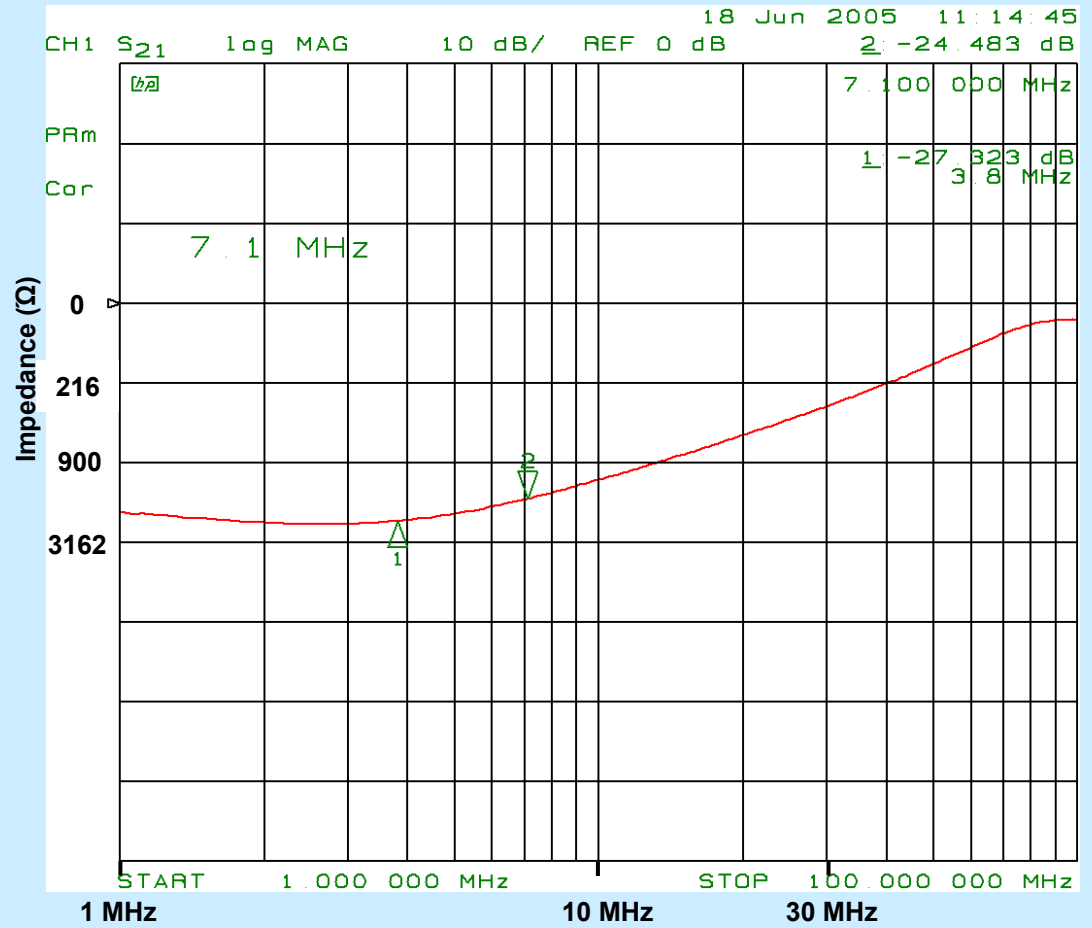


# IMPEDANCE MEASUREMENTS

(Done in frequency response mode)



2 toroids  
1 turn

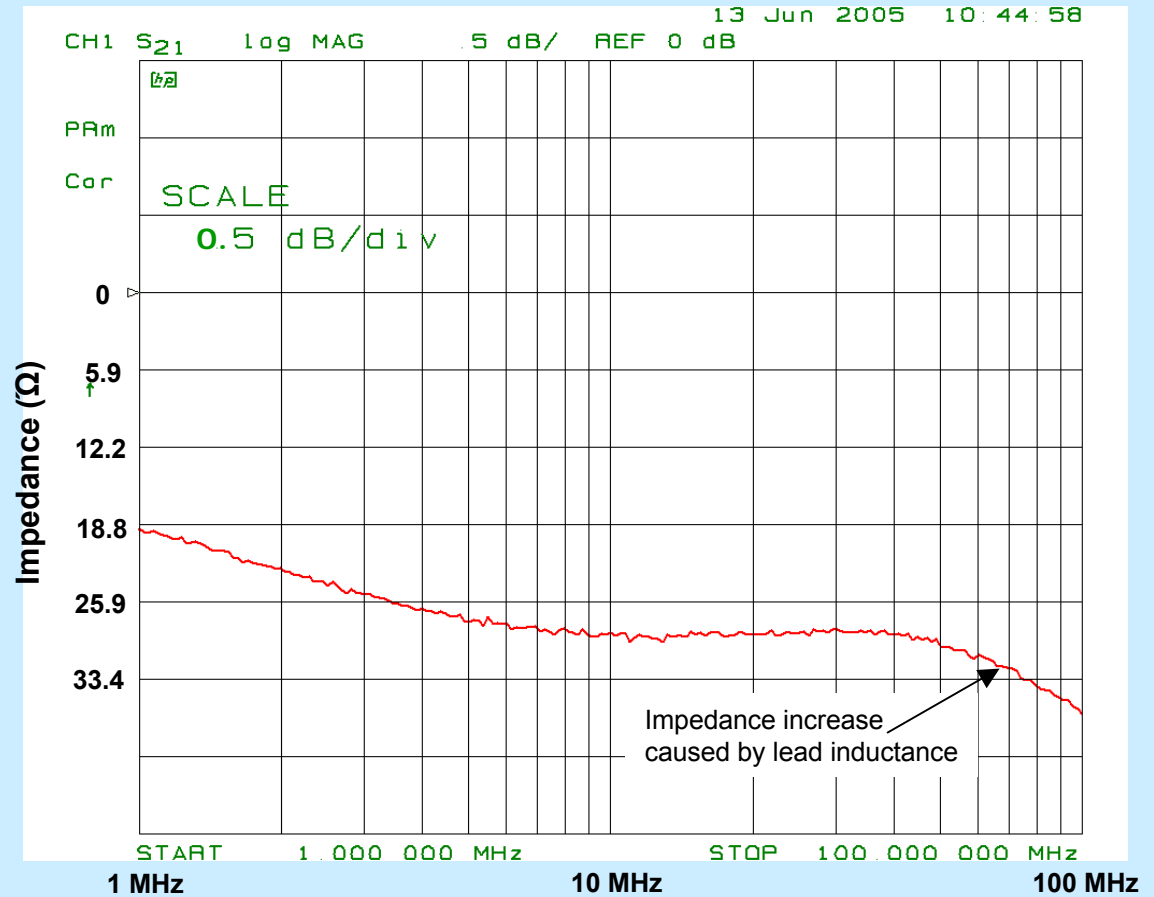


# IMPEDANCE MEASUREMENTS

(Done in frequency response mode)




2 toroids 5 turns

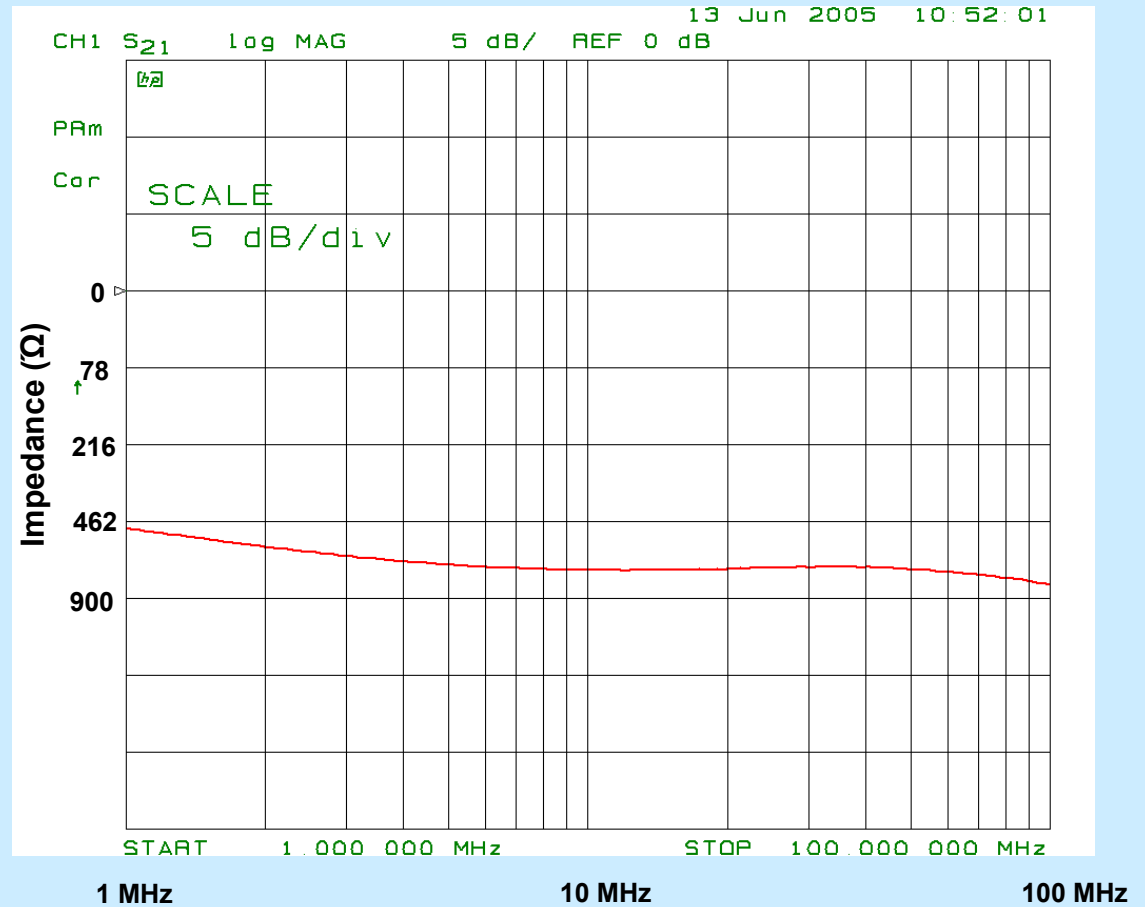

# IMPEDANCE MEASUREMENTS

(Done in frequency response mode)

Coax with 25, #43 beads

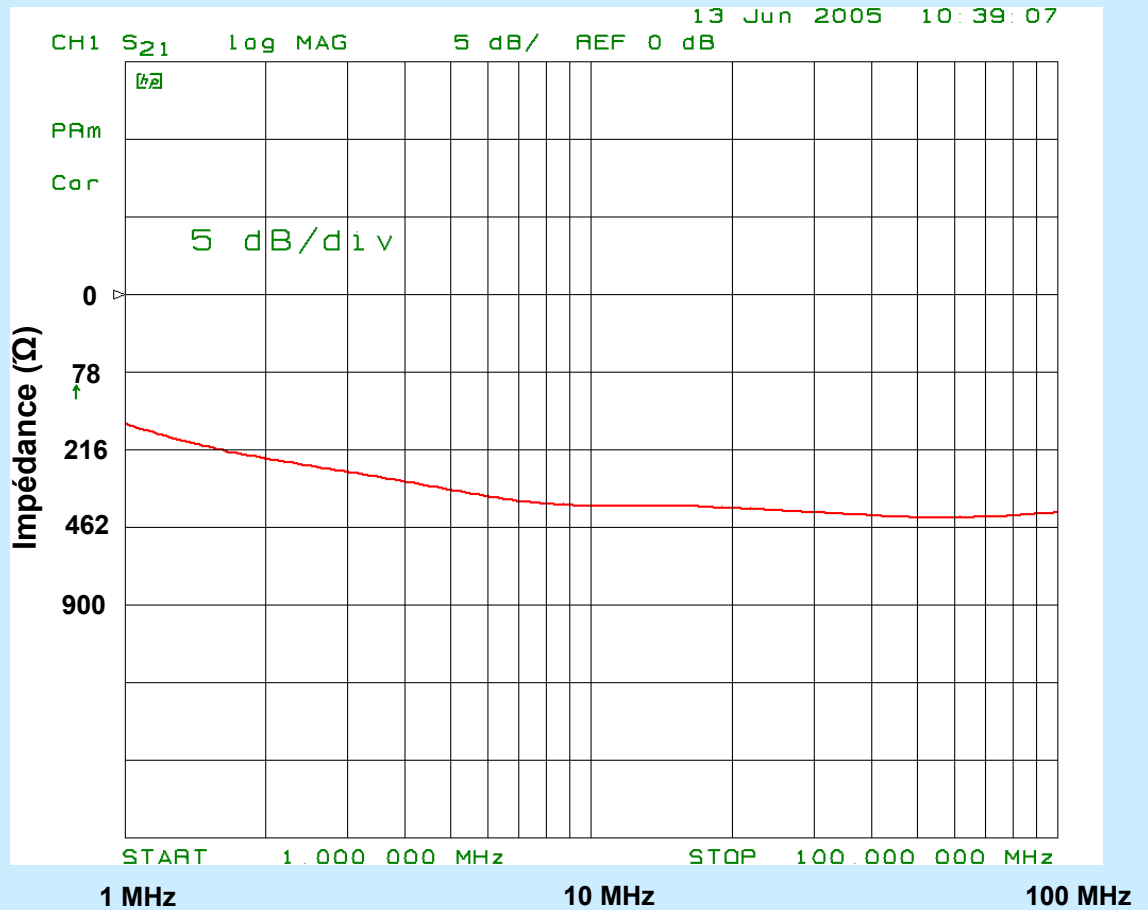


# IMPEDANCE MEASUREMENTS

(Done in frequency response mode)

#14 Wire with 50 beads #73




Excellent at HF

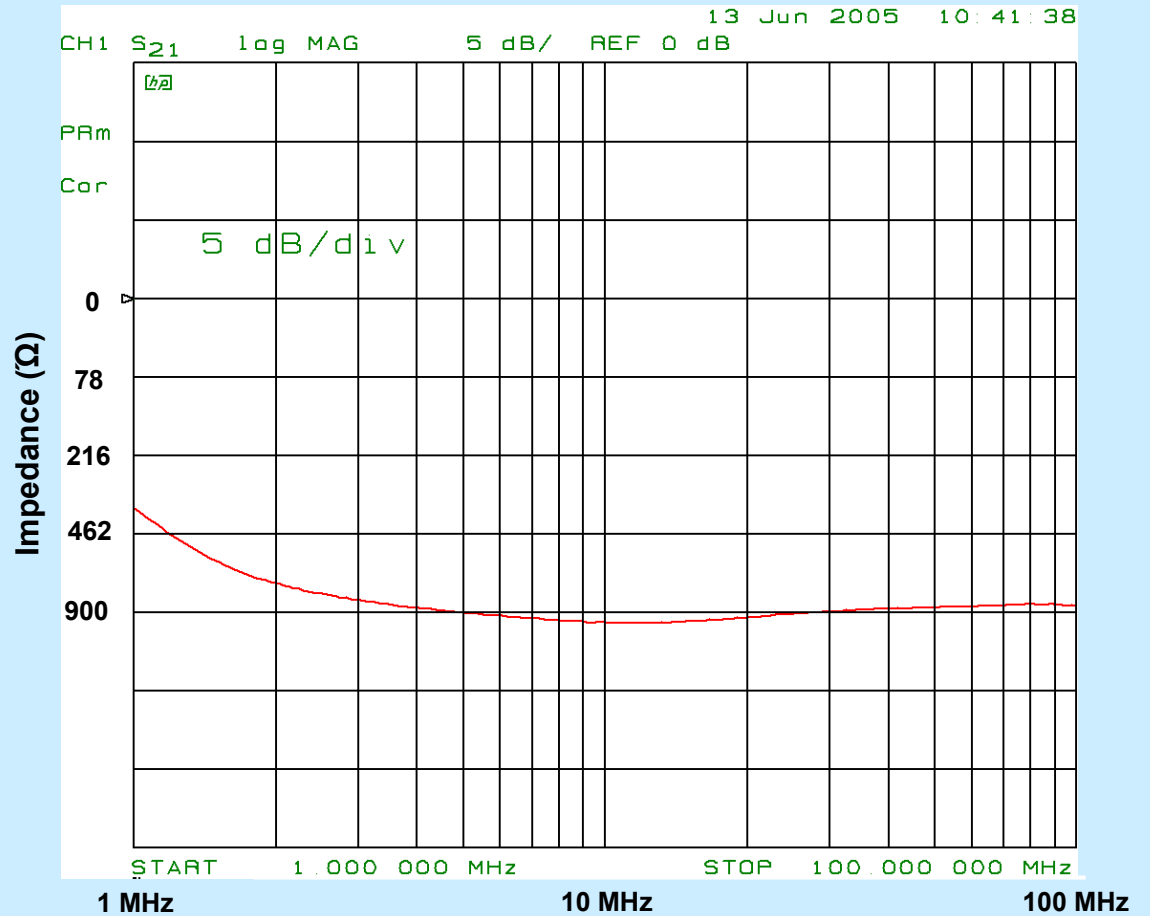


# CHECK YOUR FERRITES WITH YOUR SWR ANALYZER

## FROM SWR MEASUREMENTS

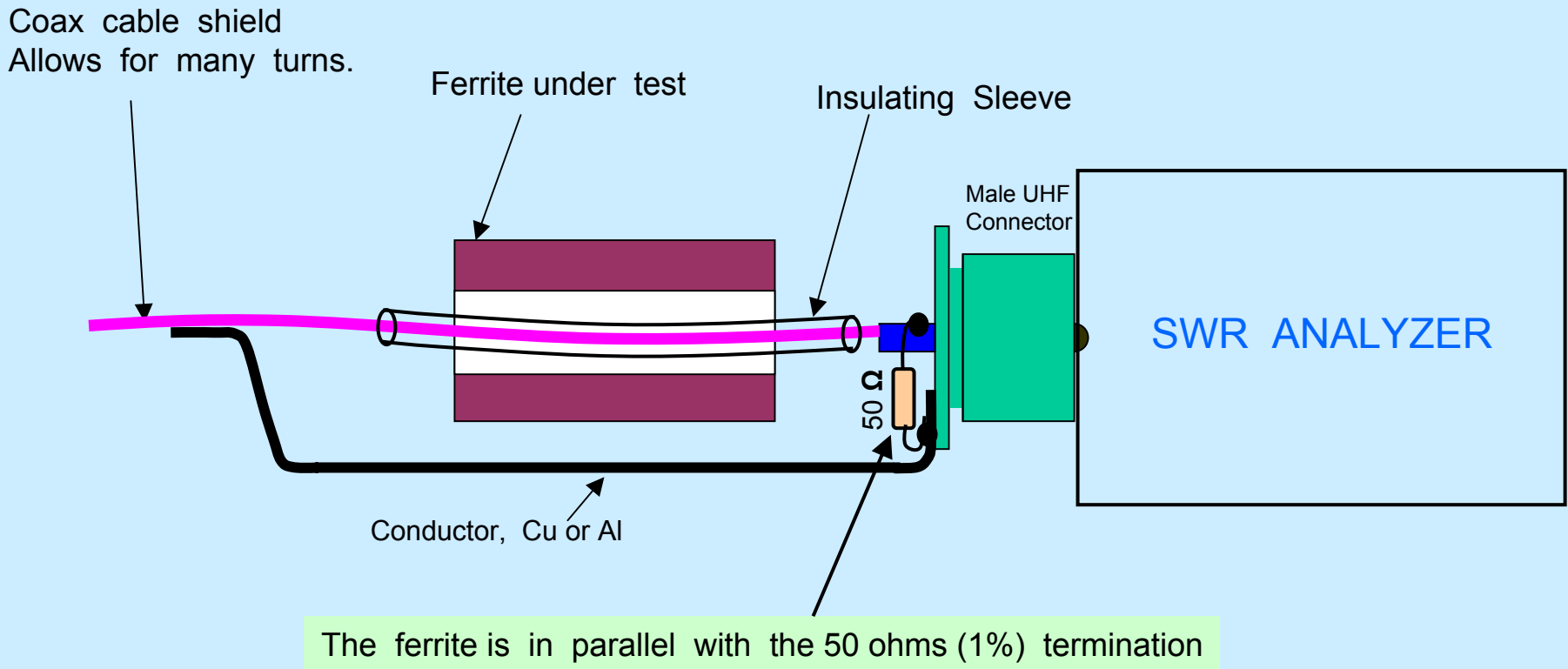


# FERRITE IMPEDANCE VS MEASURED SWR

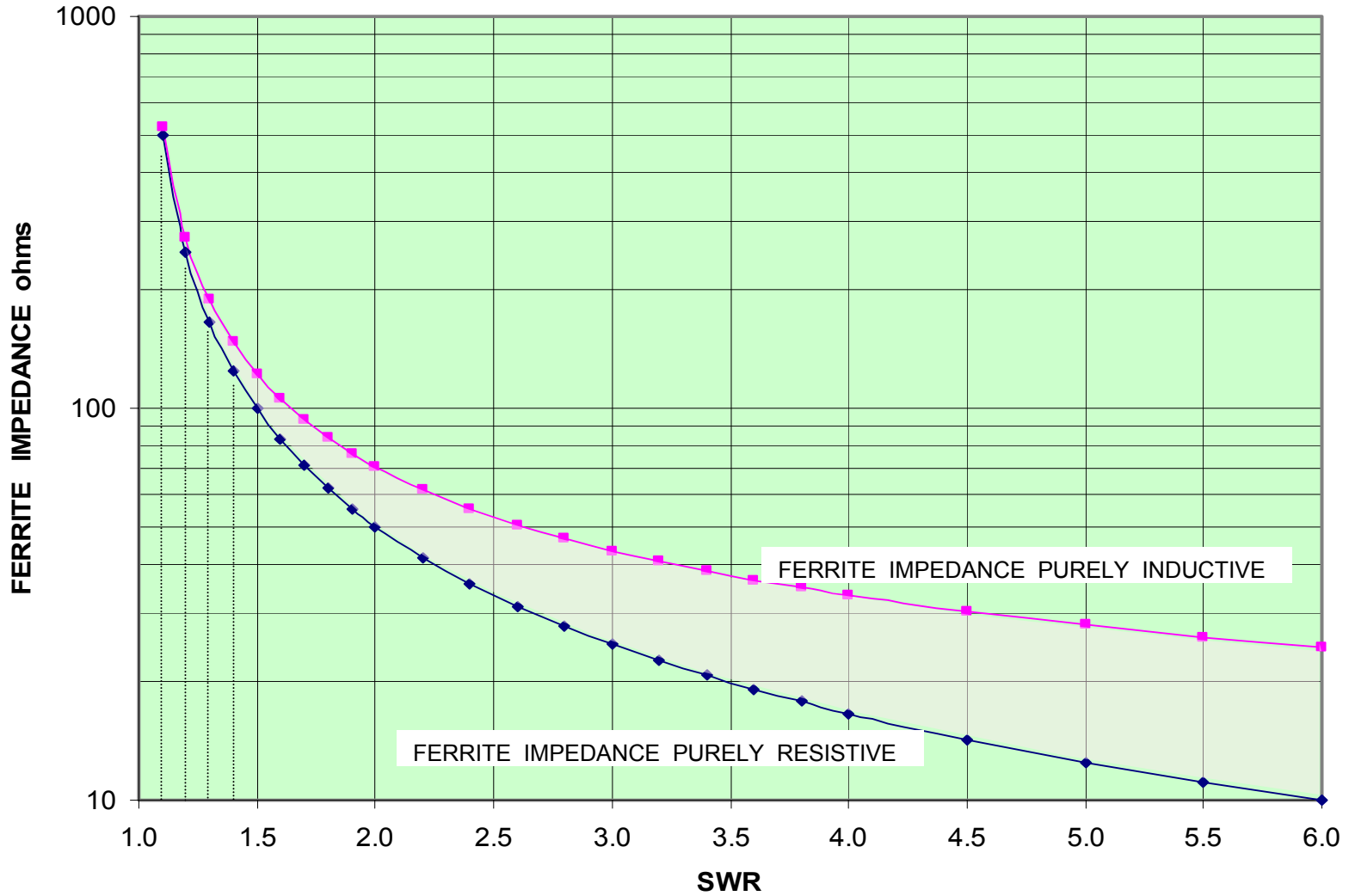

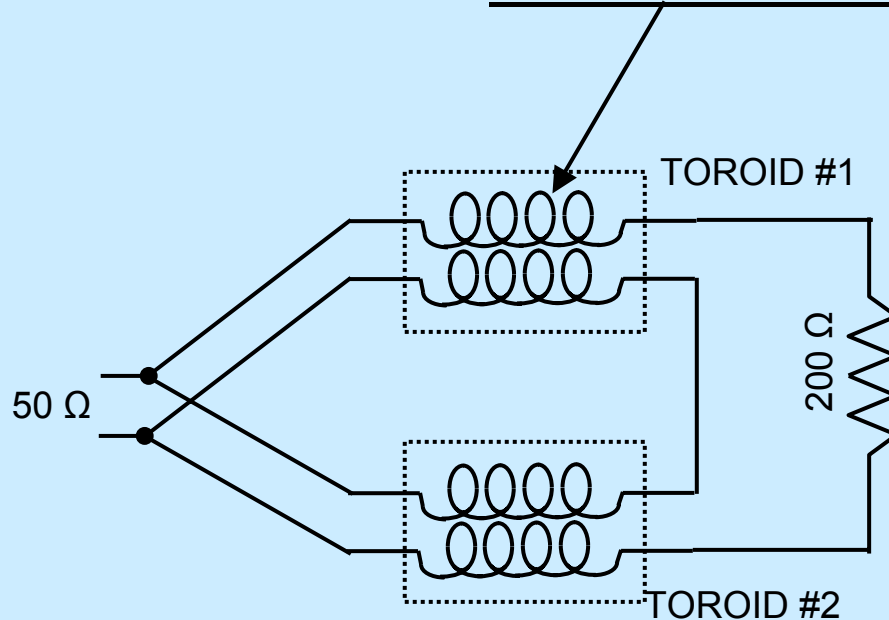
# CURRENT BALUN GIVING A 4:1 IMPEDANCE RATIO

- USES 2 PARALLEL WIRES INSTEAD OF A COAX
- MAKES A COMPACT TRANSMISSION LINE




NOTE: THIS 4:1 CURRENT BALUN  
IS SUPERIOR TO THE 4:1 VOLTAGE BALUN
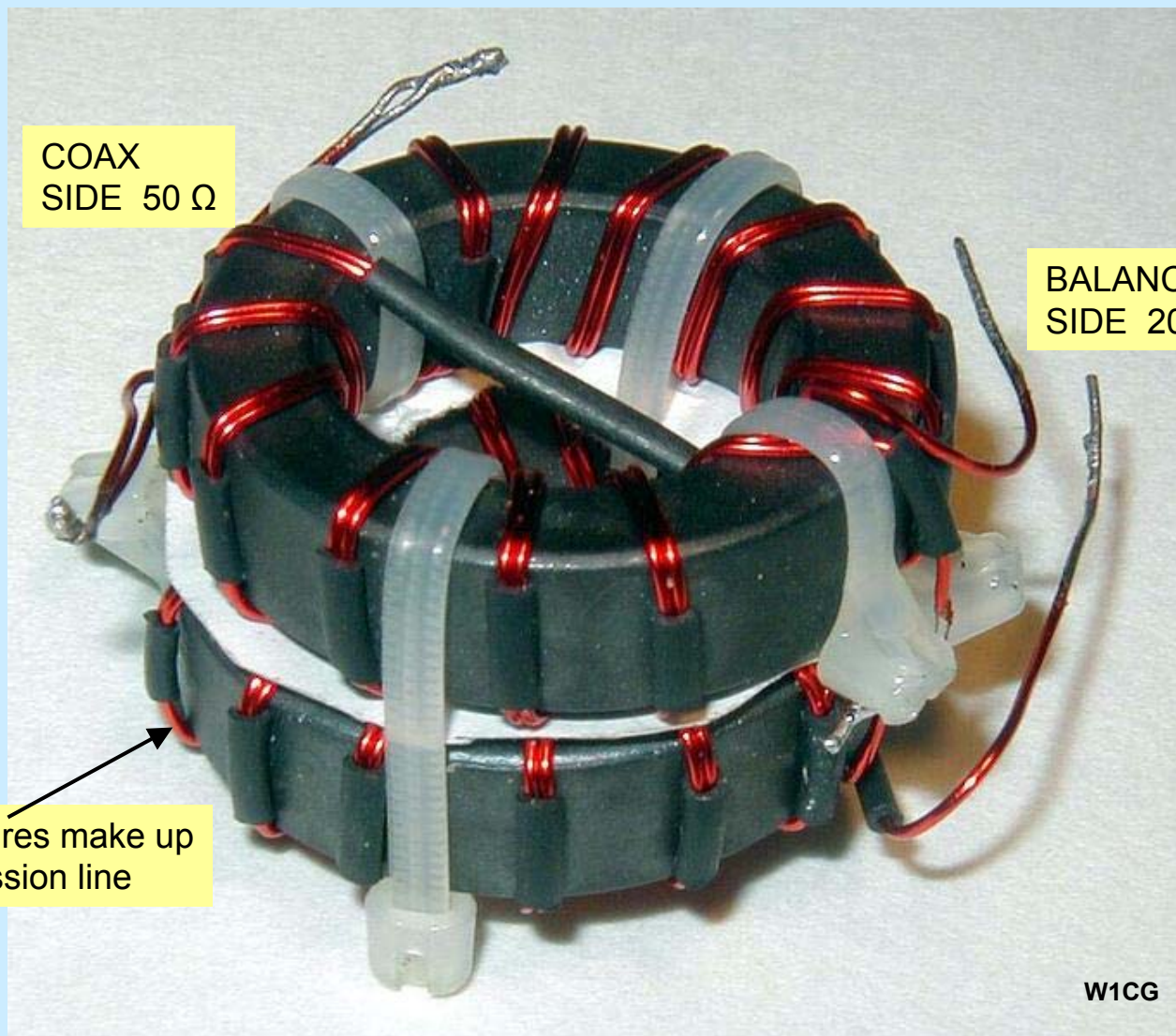
# CURRENT BALUN GIVING A 4:1 IMPEDANCE RATIO



# CURRENT MEASUREMENTS

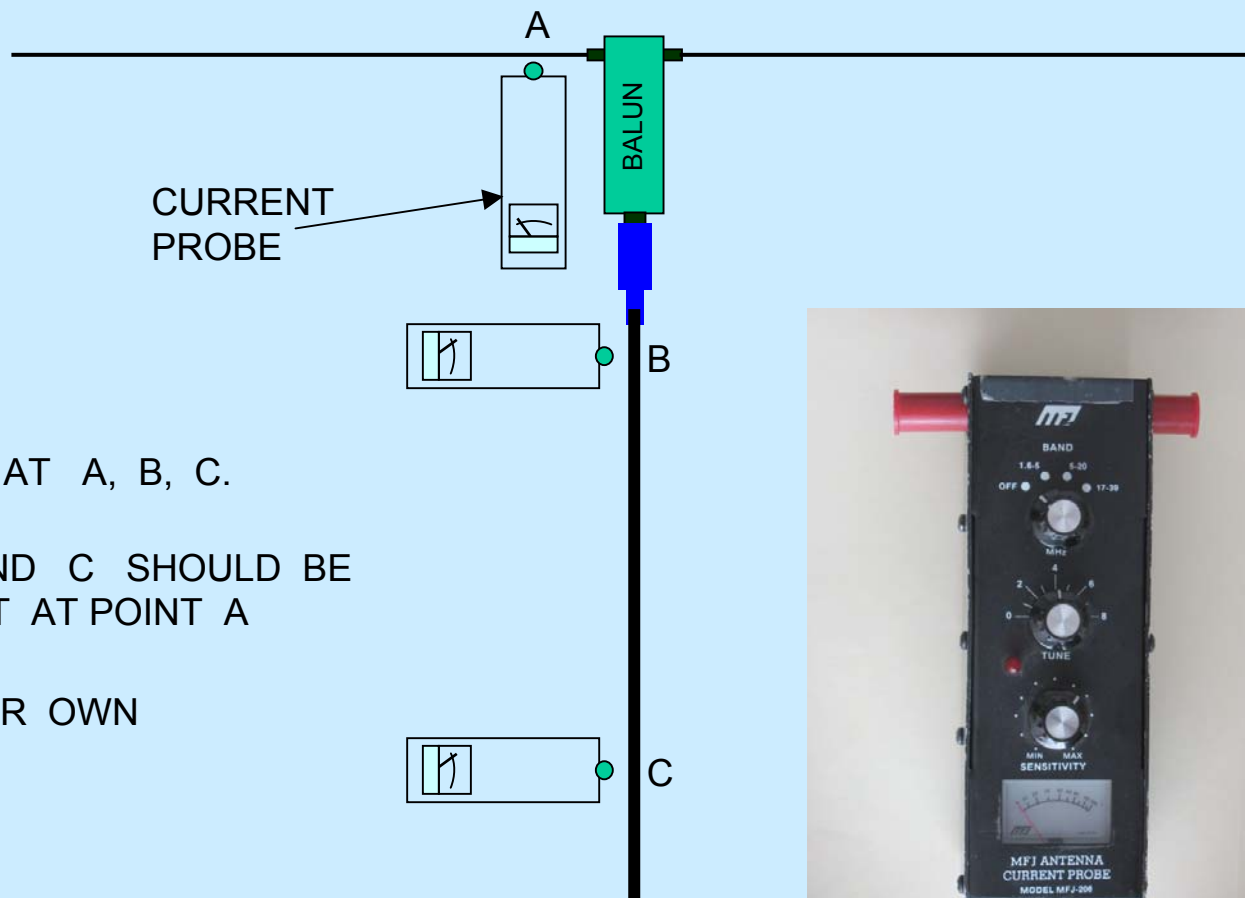

MEASURE CURRENT AT A, B, C.

CURRENTS AT B AND C SHOULD BE  
< 10% THE CURRENT AT POINT A


YOU CAN MAKE YOUR OWN  
CURRENT METER



MFJ-206
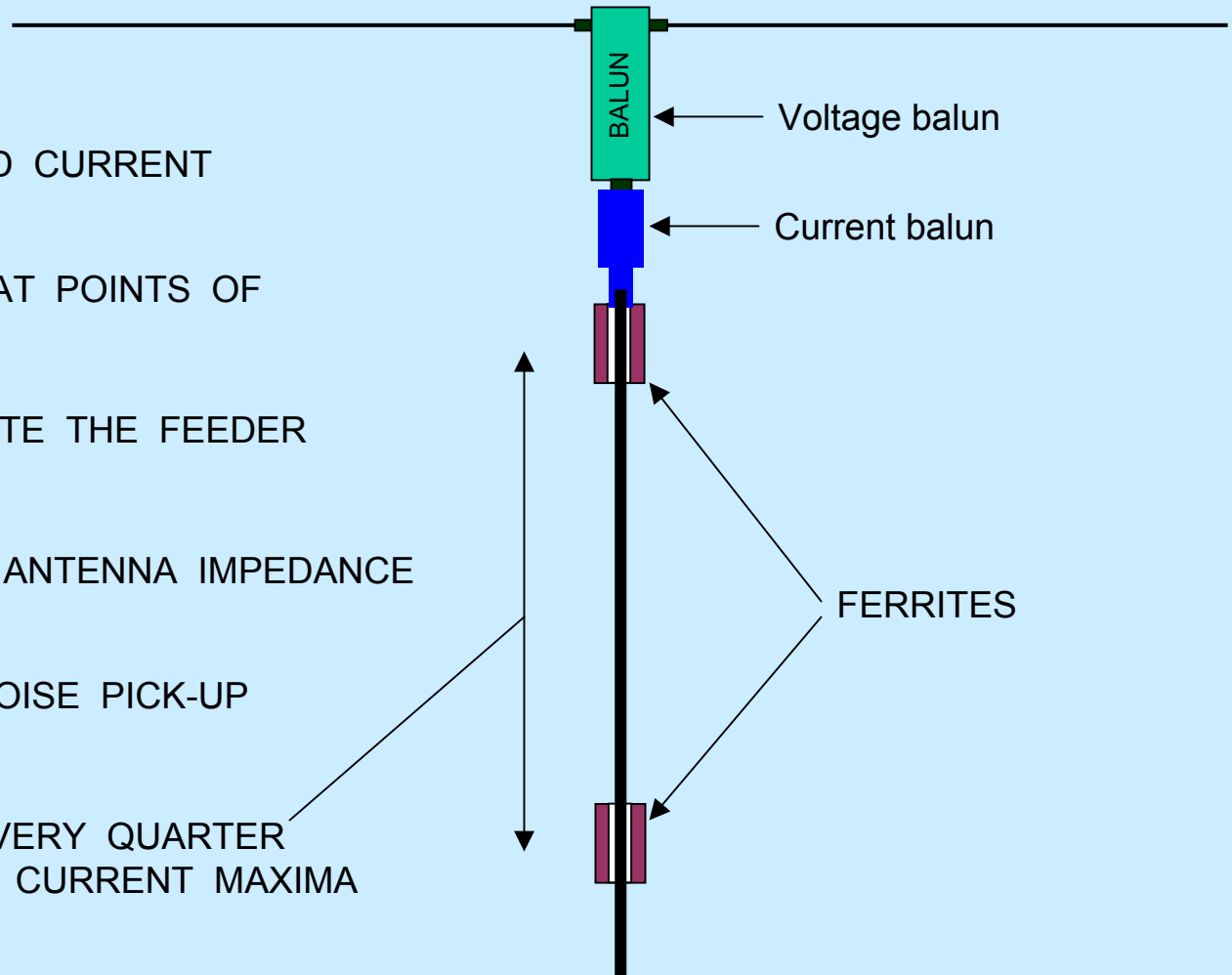
# FERRITES MAY BE USED WITH A VOLTAGE BALUN


- MEASURE THE SHIELD CURRENT
- PUT THE FERRITES AT POINTS OF MAXIMUM CURRENT
- WILL FURTHER ISOLATE THE FEEDER FROM THE ANTENNA
- WILL STABILIZE THE ANTENNA IMPEDANCE
- MAY REDUCE THE NOISE PICK-UP BY THE FEEDER
- USE FERRITES AT EVERY QUARTER WAVELENGTH OR AT CURRENT MAXIMA



# QUARTER WAVE BALUN


- A QUARTER WAVELENGTH (OR ODD MULTIPLES) SHORTED AT THE BOTTOM END WILL GENERATE A HIGH IMPEDANCE AT THE DIPOLE AND MINIMIZE COMMON MODE CURRENTS ON THE COAX OUTER SHIELD.
- USE A VELOCITY FACTOR OF 95% IN CALCULATING THE COAX LENGTH
- THIS TECHNIQUE WILL NOT WORK AT FREQUENCIES WHERE THE FEEDER IS A MULTIPLE OF  $\lambda/2$

$\lambda/4$  or odd multiples

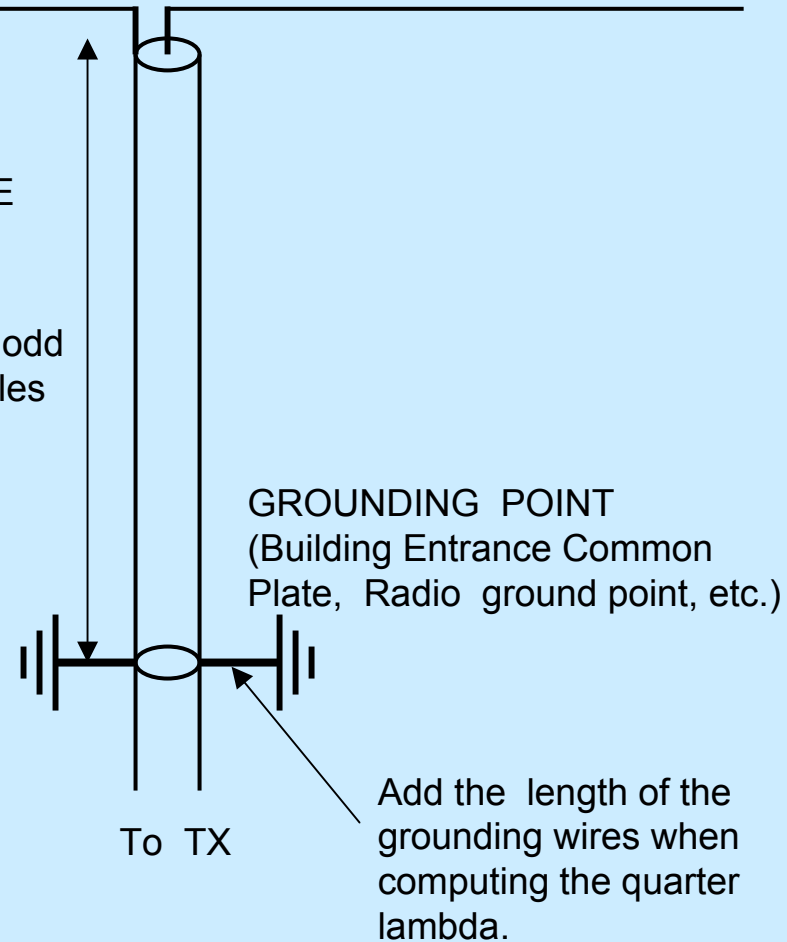

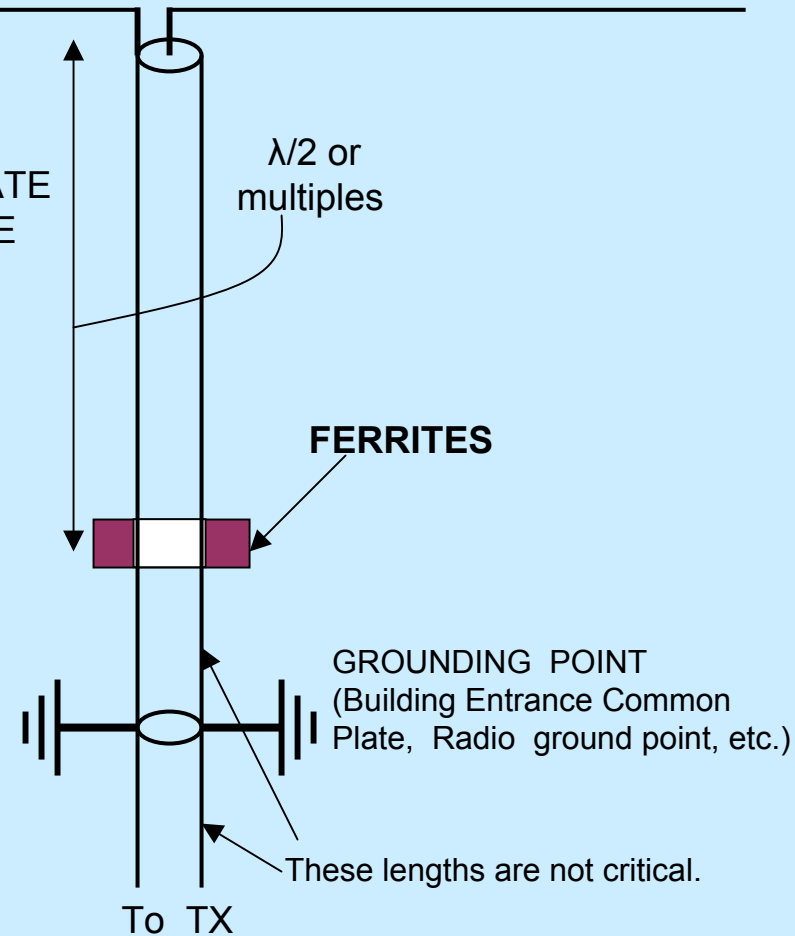
# CANNOT LOCATE BALUN AT DIPOLE FEEDPOINT: TOO HEAVY !


- SETTING THE FERRITES A HALF WAVELENGTH (OR MULTIPLES) FROM THE DIPOLE WILL GENERATE A HIGH IMPEDANCE AT THE DIPOLE AND MINIMIZE COMMON MODE CURRENTS ON THE COAX OUTER SHIELD.
- THE FERRITE IMPEDANCE SHOULD BE  $500\Omega$  OR MORE. (CHECK FOR HEATING)
- THE LENGTH BETWEEN THE TX AND THE FERRITES IS NON CRITICAL
- USE A VELOCITY FACTOR OF 95% IN CALCULATING THE COAX LENGTH



# CURRENT BALUN MADE UP OF COAX CABLE

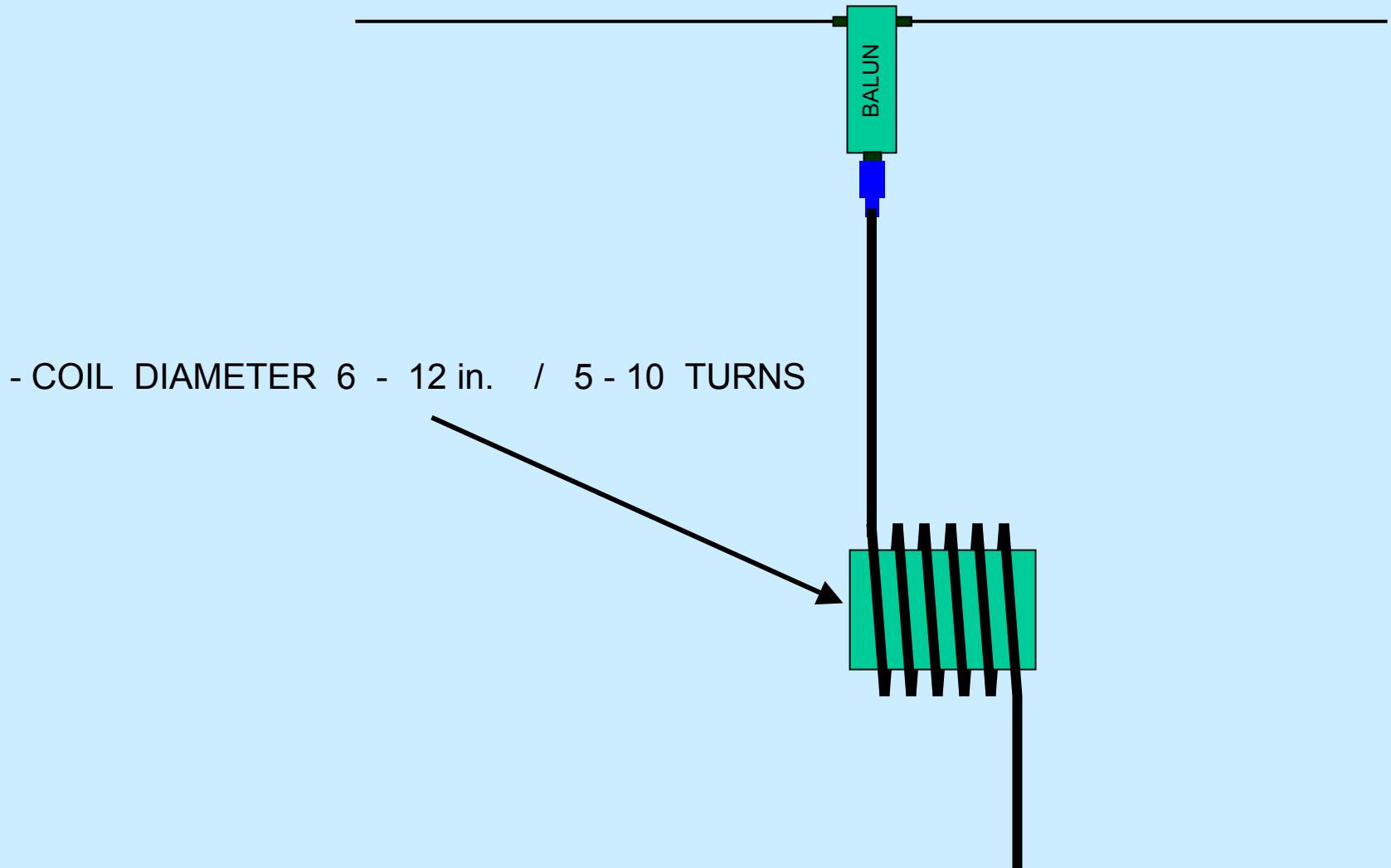


# USING A BALUN ON A VERTICAL ANTENNA

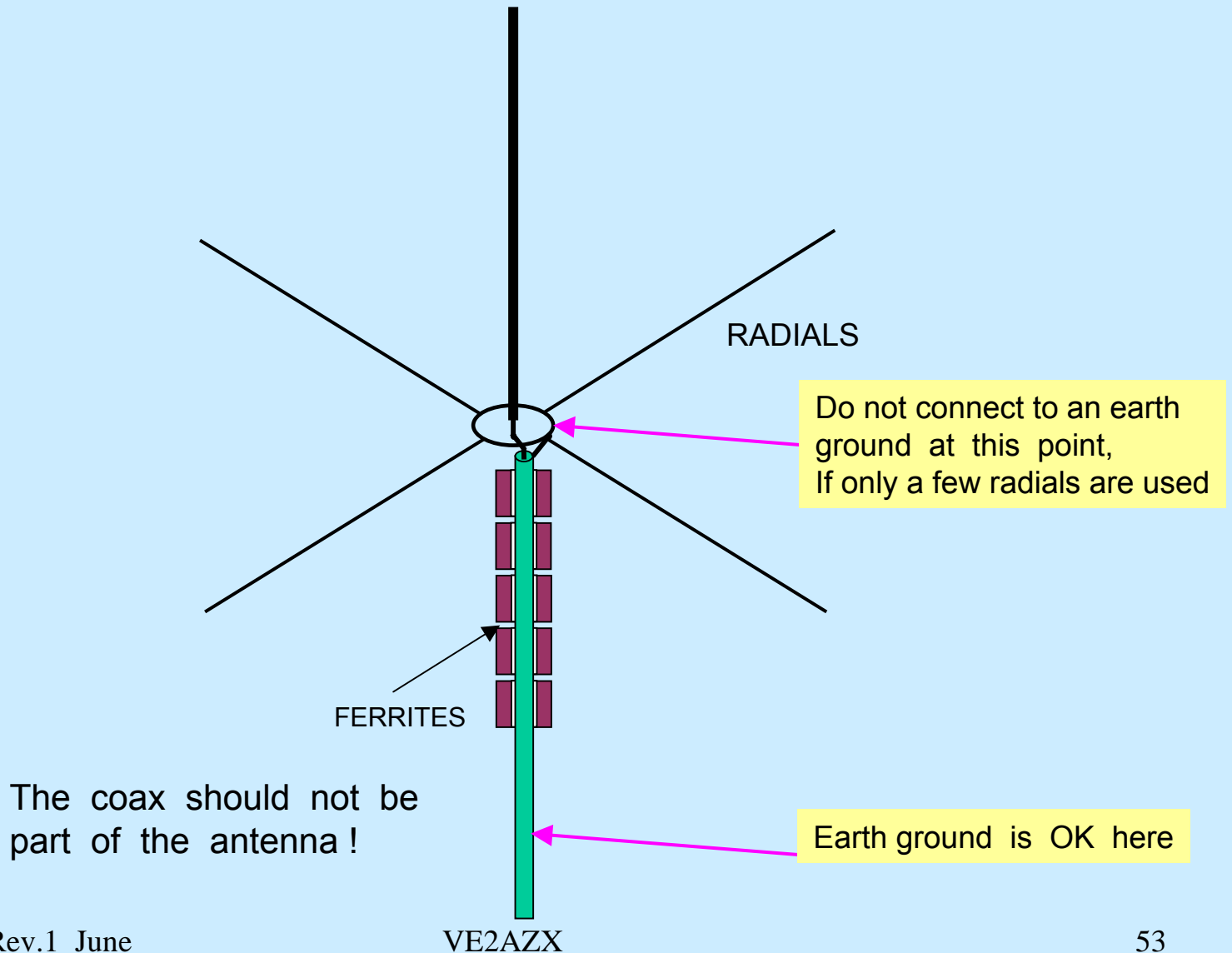

# USING FERRITES ON THE FEEDER OF VERTICAL YAGI

PREVENT INTERACTION BETWEEN COAX + MAST WITH YAGI

Ref: QEX Sept – Oct. 2006

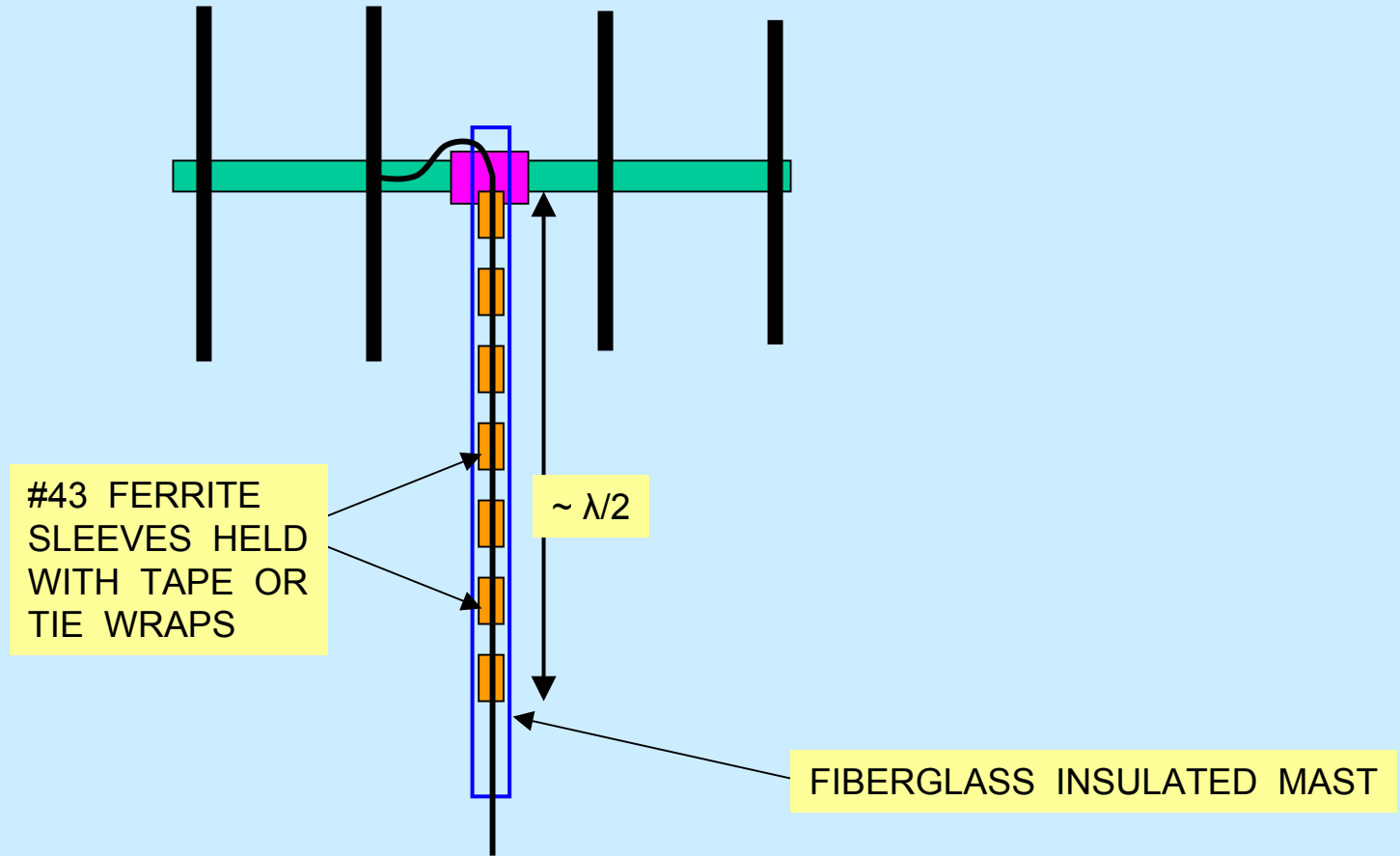


## NOTES

### - USING A BALUN UNDER HIGH SWR:

- VERIFY HEATING OF THE CORE
- DECREASE THE POWER
- USE MIX 73 ( $\mu=2500$ ) OR 31 ( $\mu=1500$ )  
FOR HIGH POWER USE MIX 43 ( $\mu=850$ ) See Ref. 4
- BALUN LOSSES MAY / WILL INCREASE UNDER HIGH SWR
- VOLTAGE BALUN NOT RECOMMENDED IF SWR > 5:1 UNLESS  
DESIGNED FOR HIGH SWR

- **BALUNS NORMALLY PROVIDE A VERY LOW ATTENUATION,  
NORMALLY < 0.3 dB ... WHEN THE LOAD IS MATCHED**

# FERRITES ARE USED EVERYWHERE

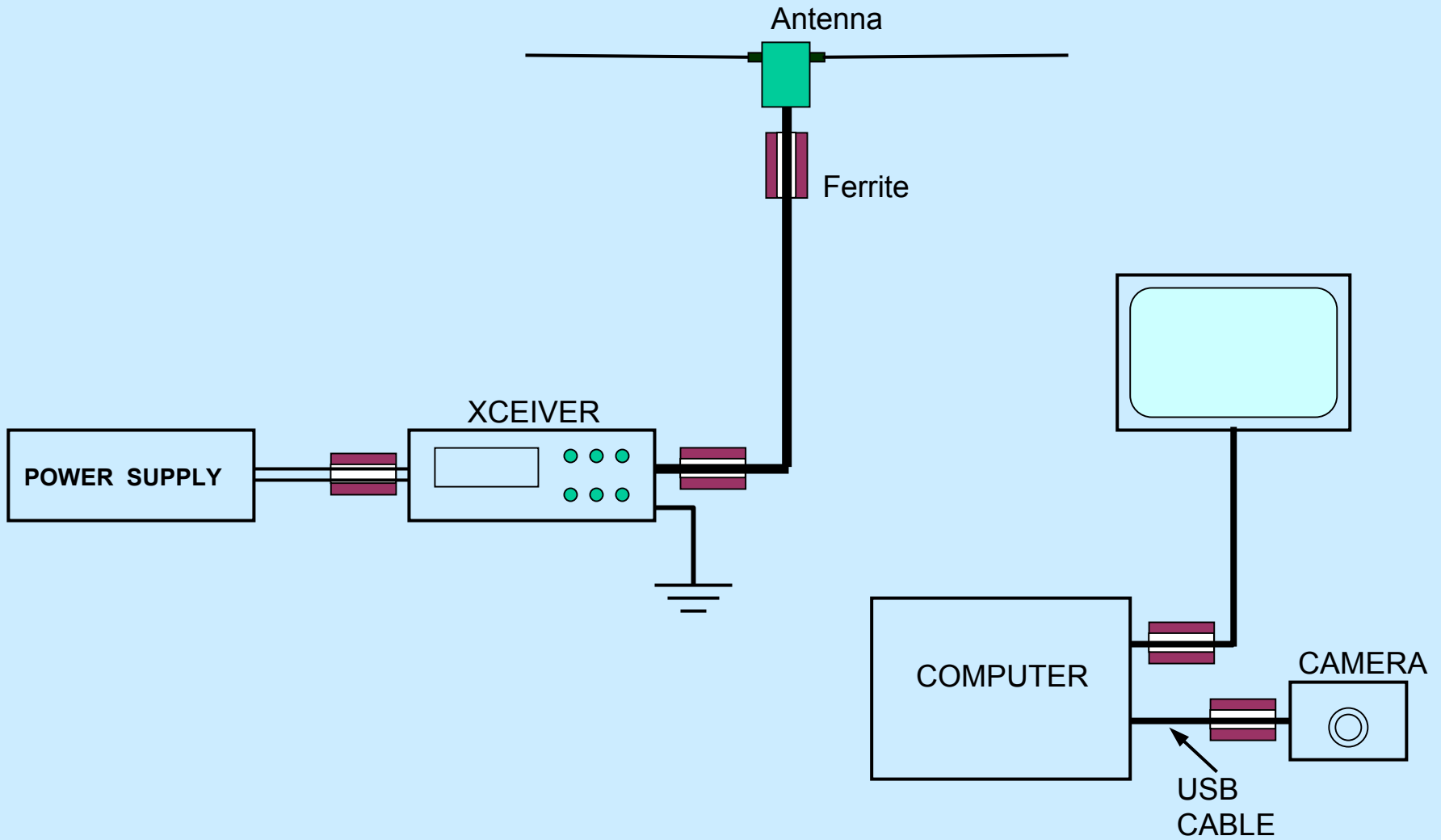

# THINGS TO REMEMBER...

- **VOLTAGE BALUNS** COVER A VERY WIDE RANGE OF IMPEDANCES
- SET EQUAL VOLTAGES AT THE OUTPUT
- GENERALLY PROVIDE NO PROTECTION AGAINST CURRENTS FLOWING ON COAX EXTERIOR
- MAY BE COMBINED WITH A CURRENT BALUN

- **CURRENT BALUNS** CREATE A AN IMPEDANCE ON THE OUTSIDE OF THE COAX (OR ANY CONDUCTOR)
- ALSO CALLED COMMON MODE CHOKES
- DECREASE COAX RADIATION AND PICK-UP
- STABILIZE THE ANTENNA IMPEDANCE
- GENERALLY 50:50 ohms RATIO (ALSO 50:200 POSSIBLE)

# THINGS TO REMEMBER...

- DECREASE COAX RADIATION ON TRANSMIT
- AND PICK-UP ON RECEIVE


## Extract from Ref. 4:

The most common reasons for using common-mode chokes are:

- (1) to reduce the fraction of the RF power that is fed to your antenna from your transmitter, but then is conducted back to your shack *via* common-mode current on your feedline, causing RFI trouble in the shack or elsewhere in your house;
- (2) to keep the transmitted RF power that 60-Hz power, telephone, TV, and other cables in the field of your antenna pick up, from bothering susceptible devices connected to these cables in your own and neighbors' houses

**Extract from Ref. 4:**

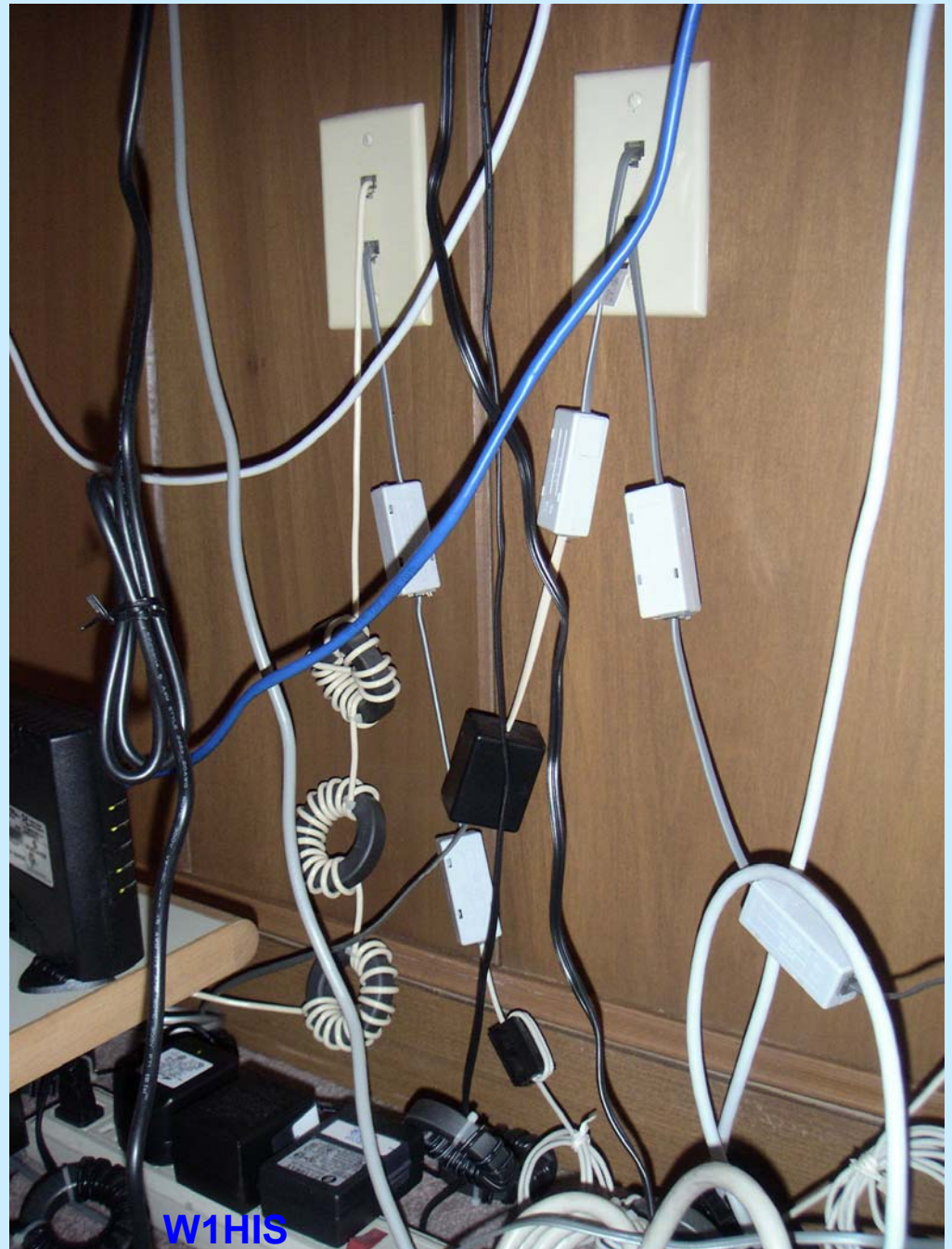(3) to keep the RF noise that all the electronic devices in your house generate, from being conducted *via* 60-Hz power, telephone and other cables to the outer shield of your radio, and from there along your feedline(s) to your antenna(s), in common-mode.



## REFERENCES

1- **W1CG Low Power Balun Kit** <http://www.njqrp.org/balun/>

2- **Transmission Line Transformers, by Jerry Sevick W2FMI**

3- **VE2AZX Web Site (this presentation):** [http://www.geocities.com/ve2\\_azx](http://www.geocities.com/ve2_azx)

4- **Chuck Counselman W1HIS :**

<http://www.yccc.org/Articles/W1HIS/CommonModeChokesW1HIS2006Apr06.pdf>

### 5- FERRITE SUPPLIERS

**Digikey** <http://www.digikey.com>

**Fair-Rite** <http://www.fair-rite.com>

**Aimdon** <http://www.amidoncorp.com>

**ByteMark** <http://www.cwsbytemark.com/prices/toroidal.php>